

Q1.a) An alarm light goes ON when a pressure sensor voltage rises above 4.00 V. The pressure sensor outputs 20 mV/kPa and has a time constant of 4.9 s. How long after the pressure rises suddenly from 100 kPa to 400 kPa does the light go ON?

Q1.b) A load cell is calibrated at 21°C and has the following deflection/load characteristic:

| | | | | | |
|-----------------|---|----|-----|-----|-----|
| Load(kg) | 0 | 50 | 100 | 150 | 200 |
| Deflection (mm) | 0 | 1 | 2 | 3 | 4 |

When used at 35°C, its characteristic changes to the following:

| | | | | | |
|-----------------|-----|-----|-----|-----|-----|
| Load(kg) | 0 | 50 | 100 | 150 | 200 |
| Deflection (mm) | 0.2 | 1.3 | 2.4 | 3.5 | 4.6 |

Determine the sensitivity coefficients

[10 pts]

Q2.a) A measurement signal has a frequency less than 1KHz, but there is unwanted noise at about 1MHz. Design a filter that attenuate the noise to 1% using a capacitor 0.01μf. What is the effect on the measurement signal at its maximum of 1KHz (give a comment on the result)?

Q2.b) Signal conditioning analysis shows that the following equation must relate output voltage to input voltage: $V_o = 3.35V_i - 2.68$. Design circuits to do this using a differential amplifier?

[12 pts]

Q3.a) Using timing diagram, explain the control lines that coordinate the operation of ADCs?

Q3.b) Design a 5-bit weighted-resistor DAC whose full-scale output voltage is -15v. Logic levels are 1=5v and 0=0v. What is the output voltage when the input is 01010?

[10 pts]

Good Luck

spring 2017

1st exam

Q2) a $f_s = 1 \text{ KHz}$, $f_n = 1 \text{ MHz}$ so use LOW pass filter

$$\frac{V_o}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$\frac{1}{100} = \frac{1}{\sqrt{1 + \left(\frac{1 \text{ MHz}}{f_c}\right)^2}} \rightarrow f_c = 10.0005 \text{ KHz}$$

$$\frac{V_o}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{1 \text{ K}}{10.0005 \text{ K}}\right)^2}} \rightarrow \frac{V_o}{V_{in}} = 0.9956377$$

$$f_c = \frac{1}{2\pi RC} \rightarrow R = \frac{1}{2\pi f_c C}$$

$$R = \frac{1}{2\pi \times 10.0005 \text{ KHz} \times 0.01 \mu\text{F}} \rightarrow R = 1.59075 \text{ K}\Omega$$

use $R = 1.5 \text{ K}\Omega$ and recalculate

$$f_c = 10.61033 \text{ KHz}$$

$$\frac{V_o}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{1 \text{ K}}{10.61033 \text{ K}}\right)^2}} \times 100\% \rightarrow \frac{V_o}{V_{in}} = 99.5588\%$$

The signal is affected by the filter and it has been attenuated, but since the noise & signal frequencies are so far of each other, the effect is so small

Q1) Temperature sensor sensitivity is $4\Omega/^\circ\text{C}$, in the range $(\pm 25^\circ\text{C})$ and its value at 0°C is 280Ω . Using Wheatstone bridge convert its range to volt, and send its value using $(4\text{mA} - 20\text{mA}$ transmitter), and prepare it for 8bit ADC with voltage reference $0-5\text{V}_{\text{ref}}$.

a) What is the digital output of ADC at the temperature -2°C . [12 pts]

Q2) Accelerometer sensor sensitivity is 0.33mA/g , used for measuring Acceleration in the range $(\pm 20\text{g})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$.

a) What is the digital output of ADC at the acceleration is -3g . [12 pts]
b) What is the acceleration when the digital output is 06H. [12 pts]

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference $(0-5\text{V})$, where: sensor output range $(-150 \sim +150\text{mV})$ with frequency 15Hz , Noise signal 20mV with frequency 150Hz , and design filter that Attenuate the noise signal to 25%, and taking in account the effect of the filter on the sensor signal. [10 pts]

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

| Temperature ($^\circ\text{C}$) | 0 | 5 | 10 | 15 | 20 |
|----------------------------------|-------|-------|-------|-------|-------|
| Resistance (Ω) | 107.6 | 109.1 | 110.2 | 111.1 | 111.7 |

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can). [4 pts]

Good Luck (Zeyad)

spring 2017


Final

Q1) $\alpha = 4 \Omega / ^\circ C$, $\pm 25^\circ C$ @ $0^\circ C = 280 \Omega$, use wheatstone bridge
 $4 \mu A \sim 20 \mu A$ transmitter , 8 bit ADC $0 \sim 5V$

Sensor output range $(\frac{4 \Omega}{^\circ C} \times 25^\circ C) + 280 \Omega \sim (25^\circ C \times \frac{4 \Omega}{^\circ C}) + 280 \Omega$

$$= (180 \Omega \sim 380 \Omega)$$

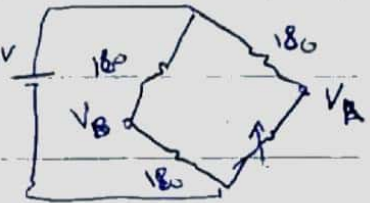use R_1 & R_2 & $R_4 = 180 \Omega$ & $V_s = 9V$



@ $-25^\circ C \rightarrow V_A = 4.5V$, $V_B = 4.5V$


$$V_o = V_A - V_B = 0V$$

@ $25^\circ C \rightarrow V_B = 4.5V$, $V_A = 9 \times \frac{380}{380 + 180} = 6.167143V$

$$V_o = V_A - V_B = V_o = 1.667143$$

bridge output range $(0V \sim 1.667143V)$

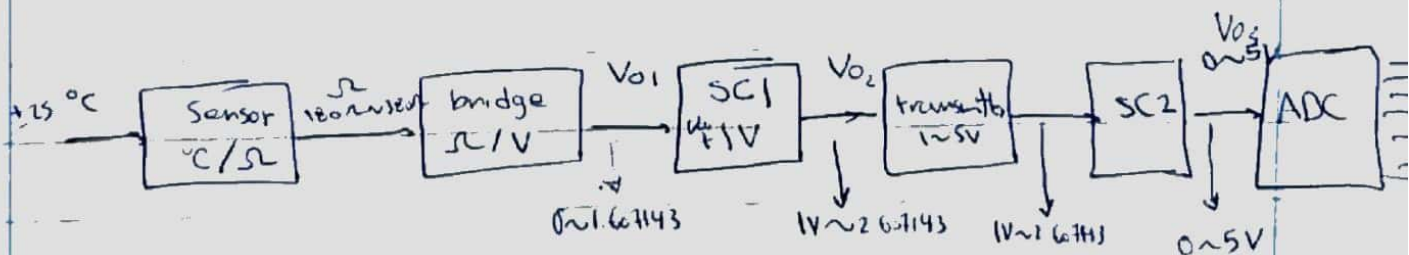use transmitter $\rightarrow mV$ $(1V \sim 2.667143V)$



$$5 = 2.607143 M + \text{offset}$$

$$0 = 1 M + \text{offset}$$

$$M = \frac{5}{1.607143} \rightarrow M = 3.111111$$

$$\text{offset} = -3.111111$$

$$V_0 = 3.111111 V_0 - 3.111111 \rightarrow \text{و نبيرو ايمونال حقيقي لارم}$$

$$\text{to find digital output @ } -2^\circ\text{C} \quad R = -284 \frac{\Omega}{^\circ\text{C}} + 280 \Omega$$

$$R = 272 \Omega, \quad V_A = 9 \times \frac{272}{272 + 180}$$

$$V_A = 5.415929 V \rightarrow \Delta V = V_0 - V_A - V_B = V_A - 4.5$$

$$V_0 = 0.915929 V \quad V_02 = V_0 + 1$$

$$V_02 = 1.915929 V, \quad V_03 = 3.111111 V_02 - 3.111111$$

$$V_03 = 2.849557 V \quad \text{Digital output} = \frac{\text{analog output}}{\Delta V}$$

$$\Delta V = \frac{5 - 0}{2^8} = 0.01953125$$

$$\text{Digital output} \approx 145 = \boxed{10010001}$$

Q2 0.33 mA/g , $\pm 20\text{g}$, 8bit ADC $\pm 4\text{V}$

accelerometer output range = $(0.33 \frac{\text{mA}}{\text{g}} \times -20\text{g} \sim 0.33 \frac{\text{mA}}{\text{g}} \times 20\text{g})$
 $= (-6.6 \text{ mA} \sim 6.6 \text{ mA})$

use $R = 1\text{K}\Omega$ to convert to volt

$(-6.6 \text{ mA} \times 1\text{K}\Omega \sim 6.6 \text{ mA} \times 1\text{K}\Omega)$

voltage output range $(-6.6\text{V} \sim 6.6\text{V})$

~~$$\begin{aligned} G &= 4 \text{ M} \text{ offset} \\ -6.6 &= -M + \text{offset} \\ M &= 1.65, \text{ offset} = 0 \\ V_{o2} &= 1.65 V_{o1} \end{aligned}$$~~

معدل الخرج

@ $-3\text{g} \rightarrow I = -0.99 \text{ mA}$, $V_{o1} = -0.99\text{V}$

$V_{o2} = -1.6335\text{V}$, $N = \frac{4 - (-4)}{2^8} = 0.03125\text{V}$

Digital output = $\frac{-1.6335 + 4}{0.03125} = 75 \rightarrow \boxed{01001011}$

$$\text{analog input } (0614)_{10} \rightarrow (1101) \rightarrow (6)_{10}$$

$$\text{Digital output} = \frac{\text{analog input} + 4}{0.3125}$$

$$V_{O2} = (6 \times 0.3125) - 4 = -3.8125V$$

$$V_{O1} = \frac{V_{O2}}{1.65} = -2.3106V$$

$$I = \frac{V}{R} \rightarrow I = -2.3106 \mu A$$

$$g = \text{acceleration} = \frac{-2.3106 \mu A}{0.33 \frac{A}{g}}$$

$$-7.001836g$$

Q2. $0.33 \mu A/g$, $\pm 20g$, 8-bit ADC $\pm 4V$

$$\text{accelerometer output range} = \left(0.33 \frac{\mu A}{g} \times -20g \sim 0.33 \frac{\mu A}{g} \times 20g \right) \\ = (-6.6 \mu A \sim 6.6 \mu A)$$

use $R = 1k\Omega$ to convert to volt

$$(-6.6 \mu A \times 1k\Omega \sim 6.6 \mu A \times 1k\Omega)$$

voltage output range $(-6.6V \sim 6.6V)$

$$4 = 6.6 M + \text{offset}$$

$$-4 = -6.6 M + \text{offset}$$

$$M = 0.606060, \text{offset} = 0$$

$$V_{O2} = 0.606060 V_{O1}$$

معدل التحويل

$$@ -3g \rightarrow I = -0.99 \mu A, V_{O1} = -0.99V$$

$$V_{O2} \approx -0.6$$

$$\Delta V = \frac{4 - (-4)}{2^8} = 0.03125V$$

$$\text{Digital output} = \frac{-0.6 + 4}{0.03125} = 108 \rightarrow \boxed{1101100_2}$$

$$\text{output } (0614)_{10} \rightarrow (1101)_2 \rightarrow 16'_{10}$$

$$\text{Digital output} = \frac{V_{O2} \text{ analog output} + 4}{0.03125}$$

$$V_{O2} = (6 \times 0.03125) - 4 = -3.8125V$$

$$V_{O1} = \frac{V_{O2}}{0.60606} = -6.290631V$$

$$I = \frac{V_{O1}}{1k\Omega} \rightarrow I = -6.290631 \mu A$$

$$g = \text{acceleration} = \frac{-6.290631 \mu A}{0.33 \frac{\mu A}{g}} = \boxed{-19.0625g}$$

Q3 $f_s = 15 \text{ Hz}$, $f_N = 150 \text{ Hz}$ Low pass filter

$$\frac{25}{100} = \frac{1}{\sqrt{1 + \left(\frac{150}{f_c}\right)^2}} \rightarrow f_c = 38.729833 \text{ Hz}$$

Use $C = 1 \text{ MF}$ Find R

$$R = \frac{1}{2\pi f_c C} \rightarrow R = \frac{1}{2\pi \times 1 \times 10^{-6} \times 38.729833} = 4109.363095 \Omega$$


use $R = 3.9 \text{ k}\Omega$

$$f_c = \frac{1}{2\pi \times 1 \times 10^{-6} \times 3900} \rightarrow f_c = 40.80896 \text{ Hz}$$

Find attenuation ratio for the signal

$$\frac{V_o}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{15}{40.80896}\right)^2}} \rightarrow \frac{V_o}{V_{in}} = 0.938603$$
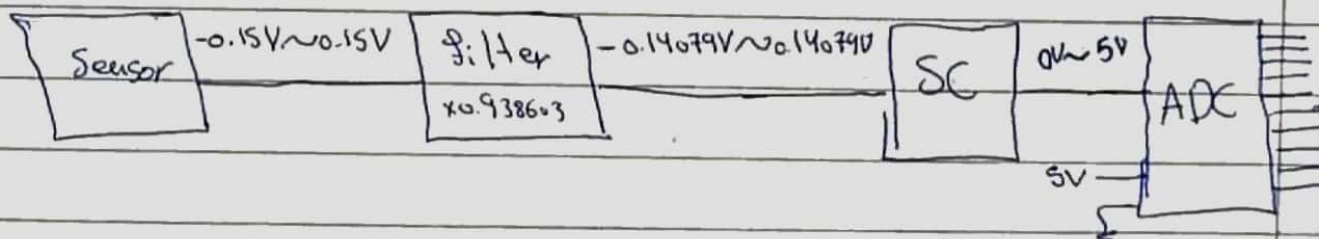
$$\begin{aligned} \text{Filter output range} &= (-0.15 \times 0.938603 \sim 0.15 \times 0.938603) \\ &= (-0.14079045 \text{ V} \sim 0.14079045 \text{ V}) \end{aligned}$$




$$5 = 0.14079045 \text{ M offset}$$

$$0 = -0.14079045 \text{ M offset}$$

$$M = 17.756886, \text{ offset} = 2.5 \quad V_o = 17.756886 V_{in} + 2.5$$

جول التحقق


| | | | |
|----------------|------------------------------------|-----|----------------------------|
| V | -0.14079045 | 0 | 0.14079045 |
| V ₀ | 29×10^{-8} ≈ 0 | 2.5 | 4.99999997 $\approx 5V$ |

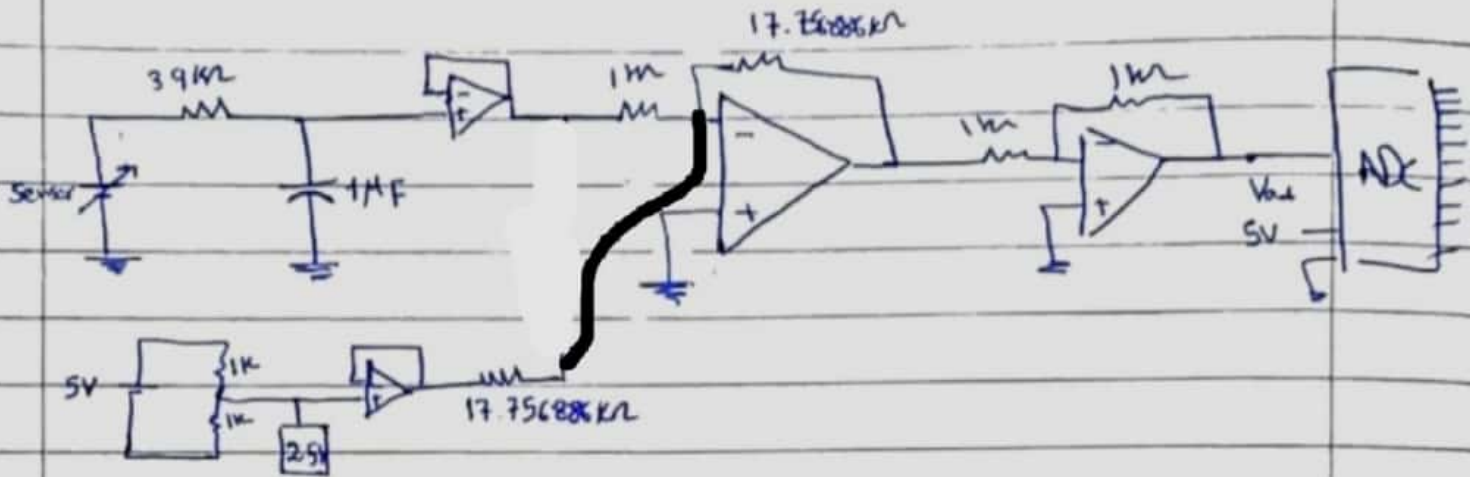

Q4) Thermo couple @ 32°C , Type J, 0°C reference

| | | | |
|---|-----|--------|---|
| L | 30° | 1.54mV | $V_M = V_L + \frac{V_H - V_L}{T_H - T_L} (T_M - T_L)$ |
| M | 32° | V_M | |
| H | 35° | 1.8mV | $V_M = 1.54 + \frac{1.8 - 1.54}{35 - 30} (32 - 30)$ |

$$V_M = 1.644mV$$

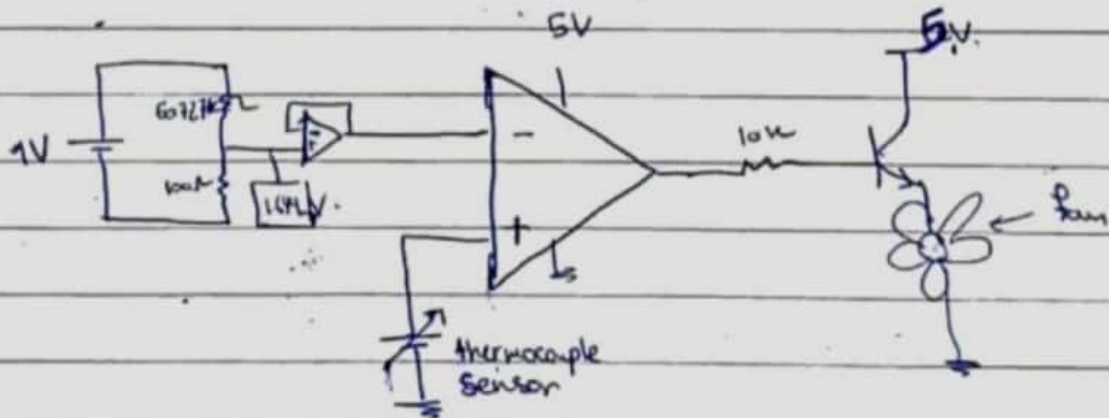

$$R(T) = R(T_0) (1 + \alpha_0 (T - T_0))$$

$$\alpha_0 = \frac{1}{R(T_0)} \frac{R_2 - R_1}{T_2 - T_1}$$


$$\begin{aligned} T_1 &= 0^\circ\text{C} & R(T_1) &= 107.6 \Omega \\ T_0 &= 10^\circ\text{C} & R(T_0) &= 110.2 \Omega \\ T_2 &= 20^\circ\text{C} & R(T_2) &= 111.7 \Omega \end{aligned}$$

$$\alpha_0 = \frac{1}{110.2} \times \frac{111.7 - 107.6}{20 - 0} \rightarrow \alpha_0 = 1.86025 \times 10^{-3}$$

$$R(13) = 110.2 (1 + 1.86025 \times 10^{-3} (13 - 10))$$

$$R(13) = 110.8149987 \Omega$$

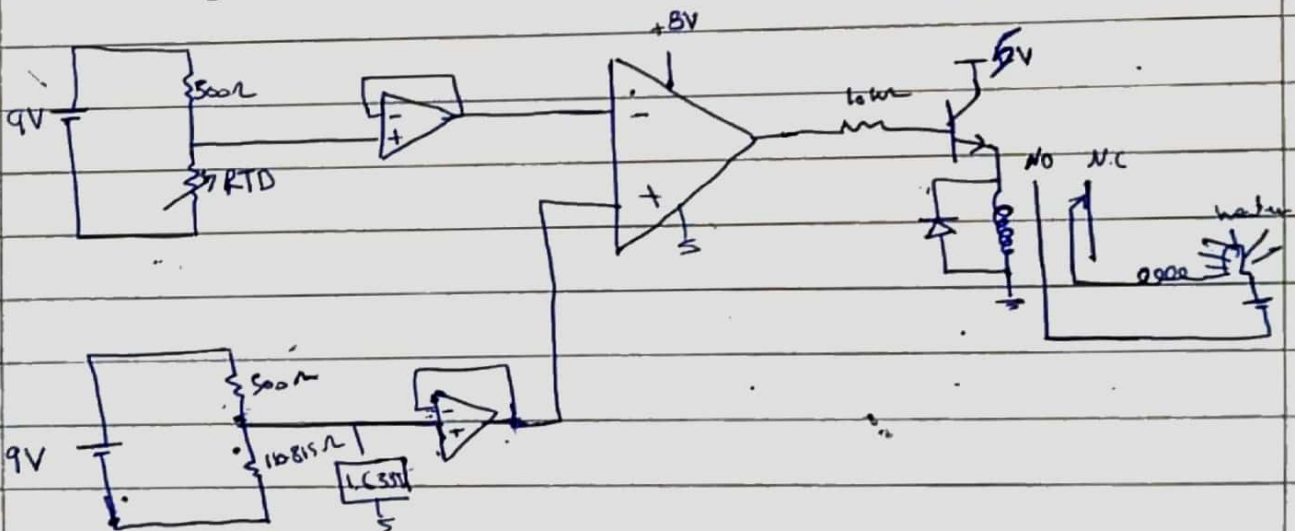Use voltage divider, $V_s = 9\text{V}$, $R = 500 \Omega$, $V = 9 \times \frac{110.8149987}{500 + 110.8149987} = 1.6327939\text{V}$



University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department

EE463

1st Exam

Time: 1:30 hr

Fall 2017

4/11/2017

- Q1) What is the basic elements of a data acquisition system, explain two of them?
- Q2) What is the difference between single ended signal and differential signal?
- Q3) A length meter range is (0 ~ 5.5m) has quoted inaccuracy of $\pm 2\%$ F.S., what is the maximum measurement error expected for this instrument in centimeter?
- Q4) What is Zero drift and sensitivity drift?
- Q5) Calculate the value of the following components:



100k = Green = 5
1000000 = Violet = 7
100 = Red = 2
1000 = orange = 3

Q6) RTD with sensitivity $3\Omega/^\circ\text{C}$, and its value = 320Ω @ 0°C , use wheatstone bridge to calculate its range in volt for temperature range (0 ~ 70°C), design s.c. circuit for ADC which voltage reference (0 ~ 4V).

-Get the temperature equation

Q7) sensitivity of pressure sensor is (2.8 mA/bar) working in the range (0 ~ 15bar), in a noisy area, design a circuit to transmit its data using (4mA ~ 20mA) transmitter, What is the new range in volt of the sensor.

Good Luck

Better 3
Be 3
Right 7
or 6
your 5
Best 4
guess 3
goes 2
very 1
wrong 0


$A, B \times 10^C$

Fall 2017 1st Exam

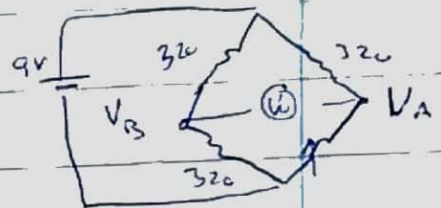Q6 35°C , @ $0^{\circ}\text{C} = 320\Omega$, $(0 \sim 70^{\circ}\text{C})$

Sensor output range $((0^{\circ}\text{C} \times \frac{3\Omega}{^{\circ}\text{C}}) + 320\Omega \sim (70^{\circ}\text{C} \times \frac{3\Omega}{^{\circ}\text{C}}) + 320\Omega)$
 $= 320\Omega \sim 530\Omega$

use R_1 & R_2 & $R_4 = 320\Omega$, $V_s = 9\text{V}$



@ $0^{\circ}\text{C} \rightarrow V_B = 4.5\text{V}$, $V_A = 4.5\text{V}$, $V_O = 0\text{V}$

@ 70°C $V_B = 4.5\text{V}$, $V_A = 9 \times \frac{530}{530 + 320} = 5.611765\text{V}$

$V_O = V_A - V_B = 1.111765\text{V}$

bridge output range $(0\text{V} \sim 1.111765\text{V})$


$4 = 1.111765\text{M} + \text{offset}$

$0 = 0\text{M} + \text{offset} \rightarrow \text{offset} = 0$

$M = 3.597883$

$V_{O2} = 3.597883 V_{O1}$

| | | | |
|----------|---|----------|----------|
| V_{O1} | 0 | 0.555883 | 1.111765 |
| V_{O2} | 0 | 2.000002 | 4.000004 |

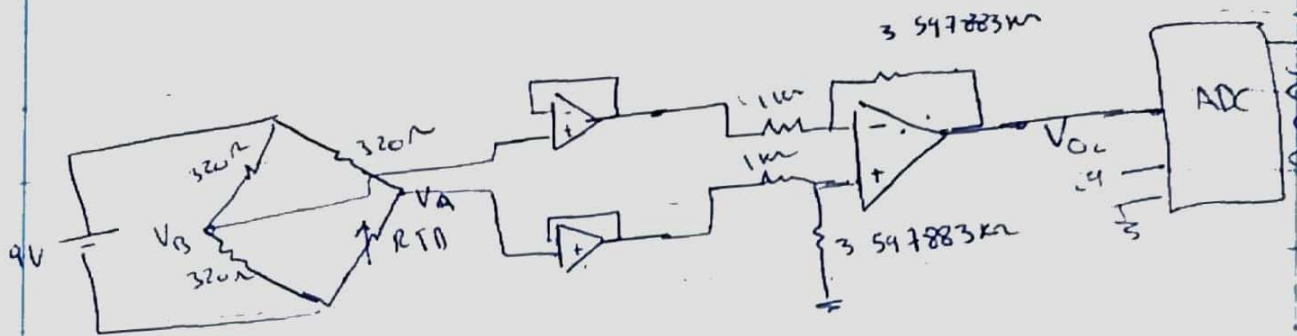

assume 8bit ADC $\rightarrow \Delta V = \frac{4}{2^8} = 0.015625V$

~~analog~~ Digital output = $\frac{\text{analog output}}{\Delta V} \rightarrow V_o = \text{Digital output} \times \Delta V$

$V_{o1} = 0.015625 \text{ Digital output}$

$V_{o1} = \frac{0.015625}{3.597883} \text{ Digital output}$

$V_{o1} = 0.00434283 \text{ D.O}$

$V_A = V_{o1} + V_B \Rightarrow V_A = 0.00434283 V_{\text{D.output}} + 4.5$

$V_A = 9 \times \frac{R_{TD}}{R_{TD} + 320} \rightarrow \frac{V_A}{9} = \frac{R_{TD}}{R_{TD} + 320}$

$R_{TD} = \frac{V_A}{9} R_{TD} + \frac{320 V_A}{9} \rightarrow R_{TD} (1 - \frac{V_A}{9}) = \frac{320}{9} V_A$

$R_{TD} = \frac{3555556 V_A}{1 - 0.111111 V_A}$

$T = \frac{\frac{3555556 V_A}{1 - 0.111111 V_A} - 320}{3}$

Q7

sensor range (0 ~ 15 bar)

sensor output range (0 ~ $\frac{2.8\text{mA}}{\text{bar}}$ ~ 15 bar ~ $\frac{2.8\text{mA}}{\text{bar}}$)


= (0 ~ 42mA)

use $R=50\Omega$ to convert to volt

voltage range = (0V ~ 2.1V)

before transmitter use S.C +1

voltage range = (1 ~ 3.1V)

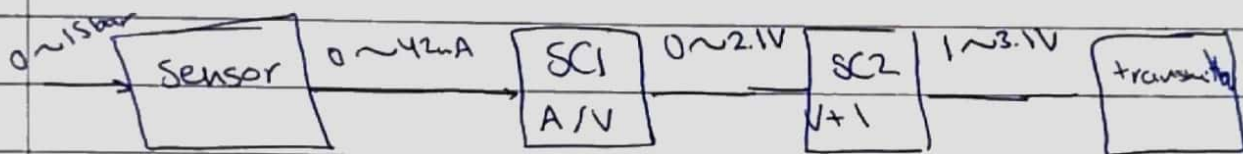


Q1) Temperature sensor sensitivity is $0.42\text{mA}/^{\circ}\text{C}$, used for temperature range $(\pm 50^{\circ}\text{C})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 3\text{V}$.

- What is the digital output of ADC at the temperature 31°C , -20°C .
- What is the temperature when the digital output is B6H. [10 pts]

Q2) Design the signal conditioning circuits to connect the sensor to 8 bit ADC with voltage reference (0-10V), where: sensor output range $(-100 \sim +100\text{mV})$ with frequency 25Hz , Noise signal 20mV with frequency 260Hz , and using filter that Attenuate the noise signal to 29% of its value, and taking in account the effect of the filter on the sensor signal. [10 pts]

Q3) Using pressure sensor which sensitivity is $2.3\text{mV}/\text{bar}$, and temperature sensor which sensitivity is $10\Omega/^{\circ}\text{C}$ and its value at zero $^{\circ}\text{C} = 300\Omega$. Design circuit which open Valve when the pressure is more than 15bar , and operate heater when temperature is less than 20°C , and operate Red LED when both of them are ON. [10 pts]

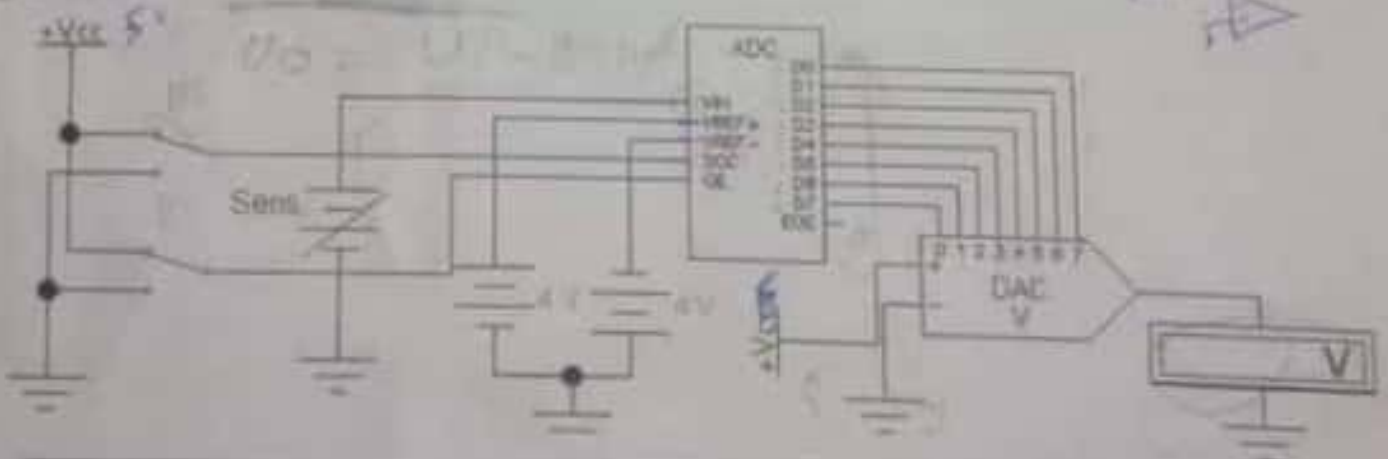Q4) What is the digital value of the ADC output and what is the analog value of DAC output at the temperature 23°C , and -30°C . Where: sensor sensitivity $= 15\text{mV}/^{\circ}\text{C}$, sensor output at $0^{\circ}\text{C} = 100\text{mV}$, sensor range $= \pm 50^{\circ}\text{C}$. [10 pts]




Good Luck (Zeyad)

Fall 2017

2nd Exam

0.42 mA/°C, ±50°C, 8bit ADC ±3V

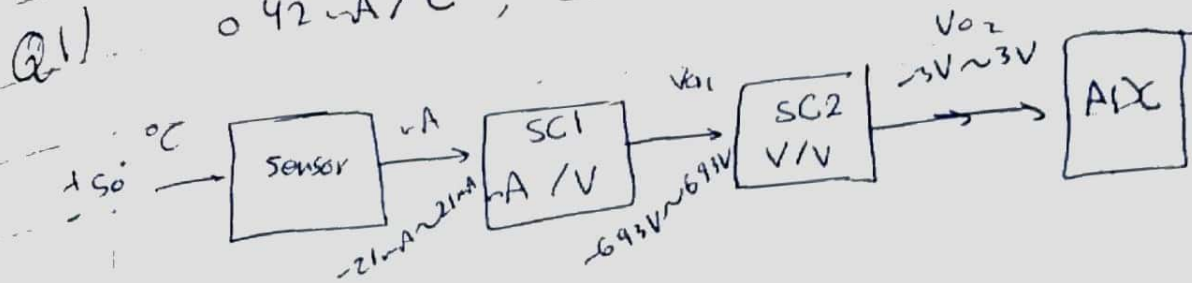

sensor output range $(-50^{\circ}\text{C} \times 0.42 \frac{\text{mA}}{^{\circ}\text{C}} \sim 50^{\circ}\text{C} \times 0.42 \frac{\text{mA}}{^{\circ}\text{C}})$

$(-21 \text{ mA} \sim 21 \text{ mA})$

use $R = 330 \Omega \rightarrow V_{o1} \text{ range } (-21 \text{ mA} \times 330 \Omega \sim 21 \text{ mA} \times 330 \Omega)$
 $= (-6.93 \text{ V} \sim 6.93 \text{ V})$

$$3 = 6.93 \text{ M} + \text{offset}$$


$$-3 = -6.93 \text{ M} + \text{offset}$$

$$M = 0.4329004$$

offset = 0

| | | | |
|----------|------------|---|-----------|
| V_{o1} | -6.93 | 0 | 6.93 |
| V_{o2} | -2.9999997 | 0 | 2.9999998 |

$$V_{o2} = 0.4329004 V_{o1}$$

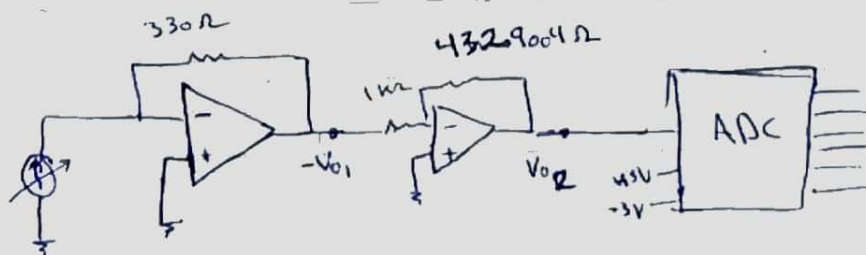

@ 3°C

$$I = 13.02 \mu A$$

$$V_{01} = 4.2966 V$$

$$V_{02} = 1.8599999 V$$

$$\Delta V = \frac{3+3}{2^8} = 0.0234375 V$$

$$\text{Digital output} = \frac{1.8599999 + 3}{0.0234375} \approx 207$$

$$= \boxed{11001111}$$

@ -20°C $\Rightarrow 76 = \boxed{01001100}$

B at $(BG)_{16} \rightarrow 182$

$$V_{02} = 1.265625 V$$

$$V_{01} = 2.923594 V$$

$$I = 8.859376 \mu A$$

$$\cancel{T = 0.021694^\circ C} \quad T = 21.0937516^\circ C$$

Q2 $f_s = 25 \text{ Hz}$ low pass filter
 $f_N = 250 \text{ Hz}$

$$\frac{29}{100} = \frac{1}{\sqrt{1 + \left(\frac{250}{f_c}\right)^2}} \rightarrow f_c = 78.785685 \text{ Hz}$$


use $C = 1 \text{ nF}$ find R

$$R = \frac{1}{2\pi \times 1 \times 10^{-6} \times 78.785685} \rightarrow R = 2.020099 \text{ k}\Omega$$

use $R = 2.2 \text{ k}\Omega$

$$f_c = \frac{1}{2\pi \times 1 \times 10^{-6} \times 2.2 \times 10^3} \rightarrow f_c = 72.343156 \text{ Hz}$$

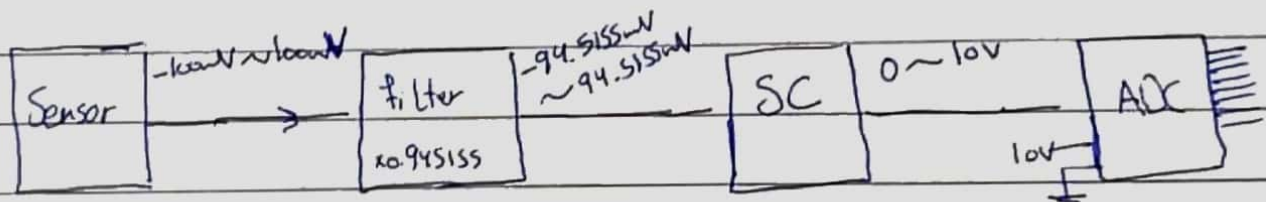attenuation ratio $\frac{V_o}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{25}{72.343156}\right)^2}} = 0.945155$



attenuated signal voltage range = $(-100\text{mV} \times 0.945155 \sim 100\text{mV} \times 0.945155)$
 $= (-0.0945155\text{V} \sim 0.0945155\text{V})$

for SC

$$10 = 0.0945155 M + \text{offset}$$

$$0 = -0.0945155 M + \text{offset} \quad M = 52.901375, \text{offset} = 5$$


~~10~~

$$V_o = 52.901375 V_{in} + 5$$

| | | | |
|----------|----------------------|---|------------|
| V_{in} | -0.0945155 | 0 | 0.0945155 |
| V_o | 9.1×10^{-8} | 5 | 9.99999991 |

$= 0$

مخطط الدارة

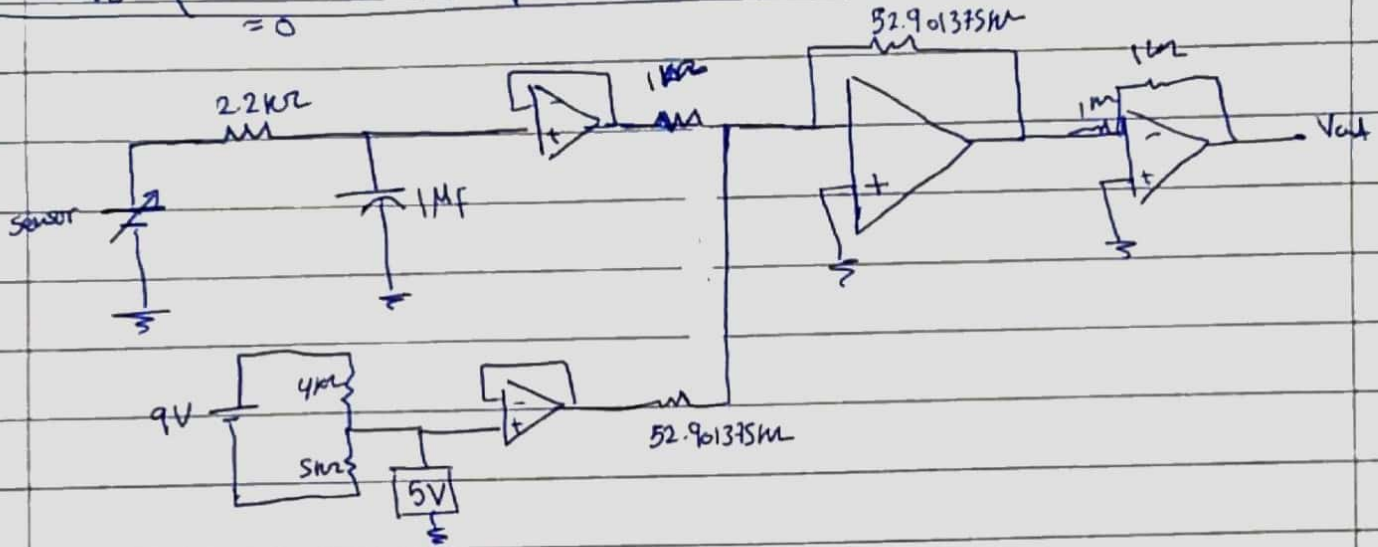

Q3)

at 15 bar

$$V = \frac{2.3 \text{ mV}}{\text{bar}} \times 15 \text{ bar}$$

$$V = 34.5 \text{ mV}$$


@ 20°C

$$R = \left(\frac{10 \Omega}{^\circ\text{C}} \times 20^\circ\text{C} \right) + 300 \Omega$$

$$R = 500 \Omega$$

use voltage divider $R_1 = 460 \Omega$ & $V_s = 9V$
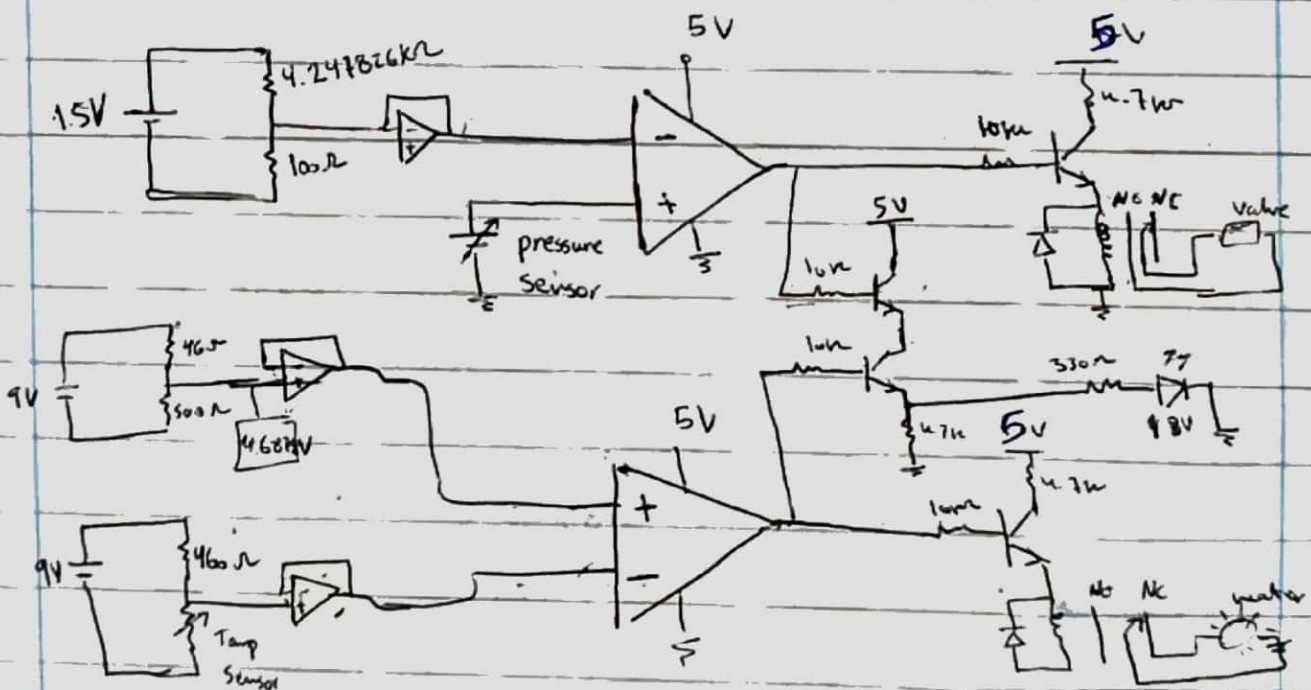
$$V_o = \frac{9 \times 500}{500 + 460} \rightarrow V_o = 4.6875V$$



Q4) at $23^{\circ}\text{C} \rightarrow V_0 = 23^{\circ}\text{C} \times \frac{15\text{mV}}{^{\circ}\text{C}} + 100\text{mV}$

$V_0 = 0.445\text{V}$

sensor ^{output} range $((-50 \times 15) + 100 \sim (50 \times 15 + 100))$

$(-0.65\text{V} \sim 0.85\text{V})$

$\Delta V = \frac{4+4}{2^8} = 0.03125\text{V}$

Digital output = $\frac{0.445 + 4}{0.03125} = 142 = \boxed{10001110}$

Digital input for DAC = $01110001 = 113$

ΔV for DAC = $\frac{5}{2^8} = 0.01953125\text{V}$

$V_0 = 113 \times 0.01953125 = \boxed{2.20703125\text{V}}$

@ -30°C $V_0 = -0.35\text{V}$

Digital output = $116 \rightarrow \boxed{01110100}$

Digital input DAC = $00101110 = 46$

$V_0 = 0.8984375\text{V}$

University of Tripoli - Faculty of Engineering

Electrical & Electronic Engineering Department

EE463

1st Exam

Time: 1:30 hr

spring 2018

20/12/2018

Q1) What elements of data acquisition system, explain two of them

Q2) Temperature sensor which sensitivity = $0.11 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$ for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12V.

A- Design circuit to send the sensor output for long distance and for ADC ($V_{\text{ref}} 0-4\text{V}$).


B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88H?

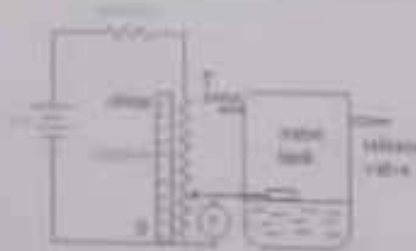Q3) Sensor used to measure pressure in range (0-30 bar) with sensitivity (7mV/bar), RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp) is more than 49°C or pressure is more 10 bar or level is less than 33cm

B- Turn ON release valve if pressure is more than 15 bar.




Good Luck (Zeyad Hamza)

Spring 2018

1st

Q2 $\beta = 0.11 \text{ mA}/^\circ\text{C}$ @ $I_C = 5 \text{ mA}$ $\pm 4^\circ\text{C}$ $R = 150 \Omega$
 $V_s = 12 \text{ V}$

a)

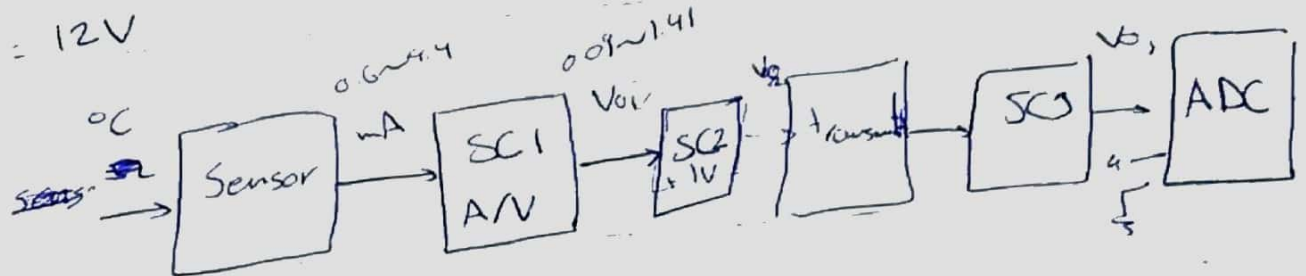

sensor output range ($0.6 \text{ mA} \sim 9.4 \text{ mA}$)

$R = 150 \Omega$

SC1 output range (voltage) = $(0.9 \text{ V} \sim 1.41 \text{ V})$

SC2 $\rightarrow V_{02} = 1 + V_{01}$

SC2 output range ($1.09 \text{ V} \sim 2.41 \text{ V}$)


SC3 $4 = 2.41 \text{ V} + \text{offset}$

$0 = 1.09 \text{ V} + \text{offset}$

$M = 3.030303$ offset = -3.3030303

$V_{03} = 3.030303 V_{02} - 3.3030303$

| | | | |
|----------|------|------|------|
| V_{02} | 1.09 | 1.75 | 2.41 |
| V_{03} | 0 | 2 | 4 |

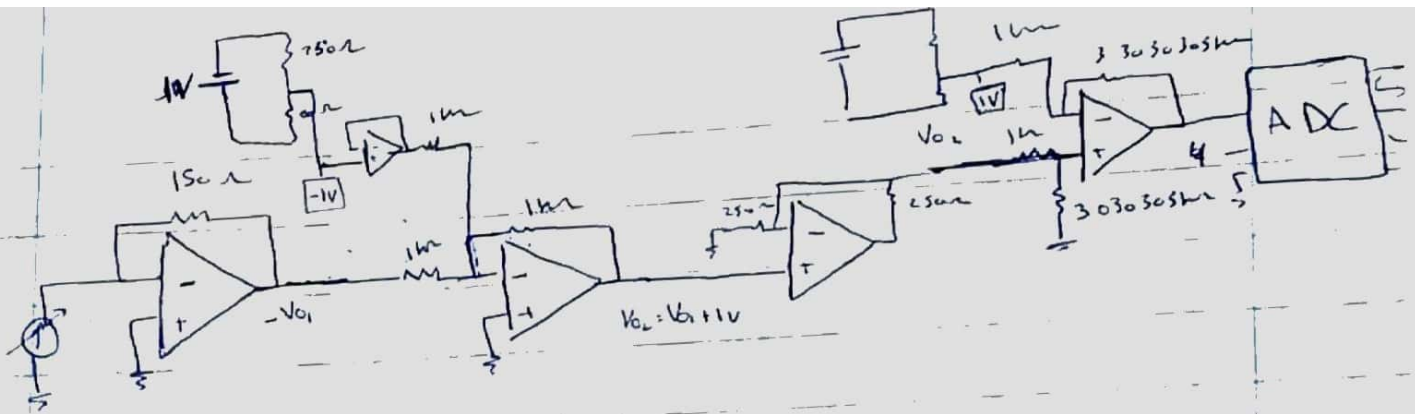

B @ $33^{\circ}\text{C} \rightarrow V_{03} = \cancel{72.0\text{V}} \quad 3.65\text{V}$

$$\Delta V = \frac{4}{2^8} = 0.015625$$

Digital output = 233 \rightarrow 11101001

@ -14 $\rightarrow V_{03} = 1.3\text{V}$

Digital output = 83 \rightarrow 01010011

C $88\text{H} \rightarrow (136)_{10}$

$V_{03} = 2.125\text{V} \rightarrow 2.5^{\circ}\text{T}$

Q3) For tank use $V_s: 12V$, $R_s = 400\Omega$, $R_{pot} = 52k\Omega$, $h_{tank} = 50cm$

1) For pressure sensor @ 6 bar

$$V = 6 \text{ bar} \times \frac{7mV}{\text{bar}} = \boxed{70mV}$$

2) For RTD PT100 @ $49^\circ C$

$$R = 49^\circ \times 0.39 \frac{\Omega}{^\circ C} + 100\Omega \rightarrow R = 119.11\Omega$$

use voltage divider $V_s = 9V$, $R_1 = 500\Omega$

$$V = 9 \times \frac{119.11}{119.11 + 500} \rightarrow \boxed{V = 1.731502V}$$

3) For the tank

$$0cm \rightarrow 0V$$



$$50cm \rightarrow 12 \times \frac{5.2}{52 + 0.4} = 11.14285714V$$



$$\text{so } S = \frac{11.14285714V}{50cm} = 0.222857V/cm$$

$$\text{@ } 33cm \rightarrow V = 0.222857 \times 33 = \boxed{7.354281V}$$

for B: @ 15 bar
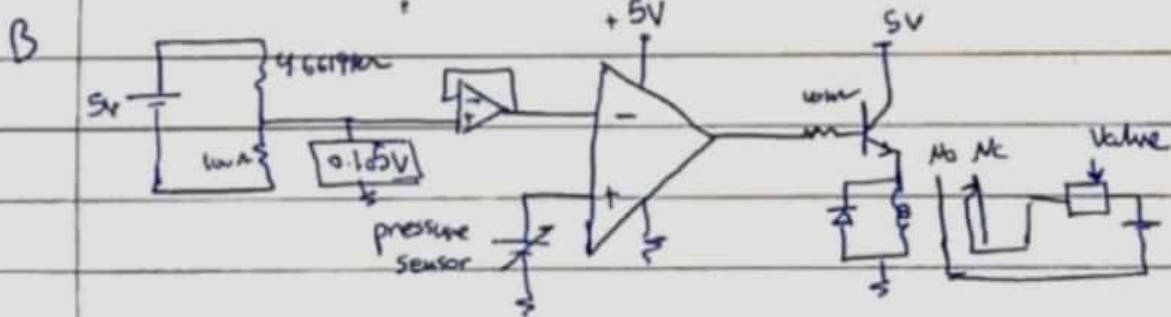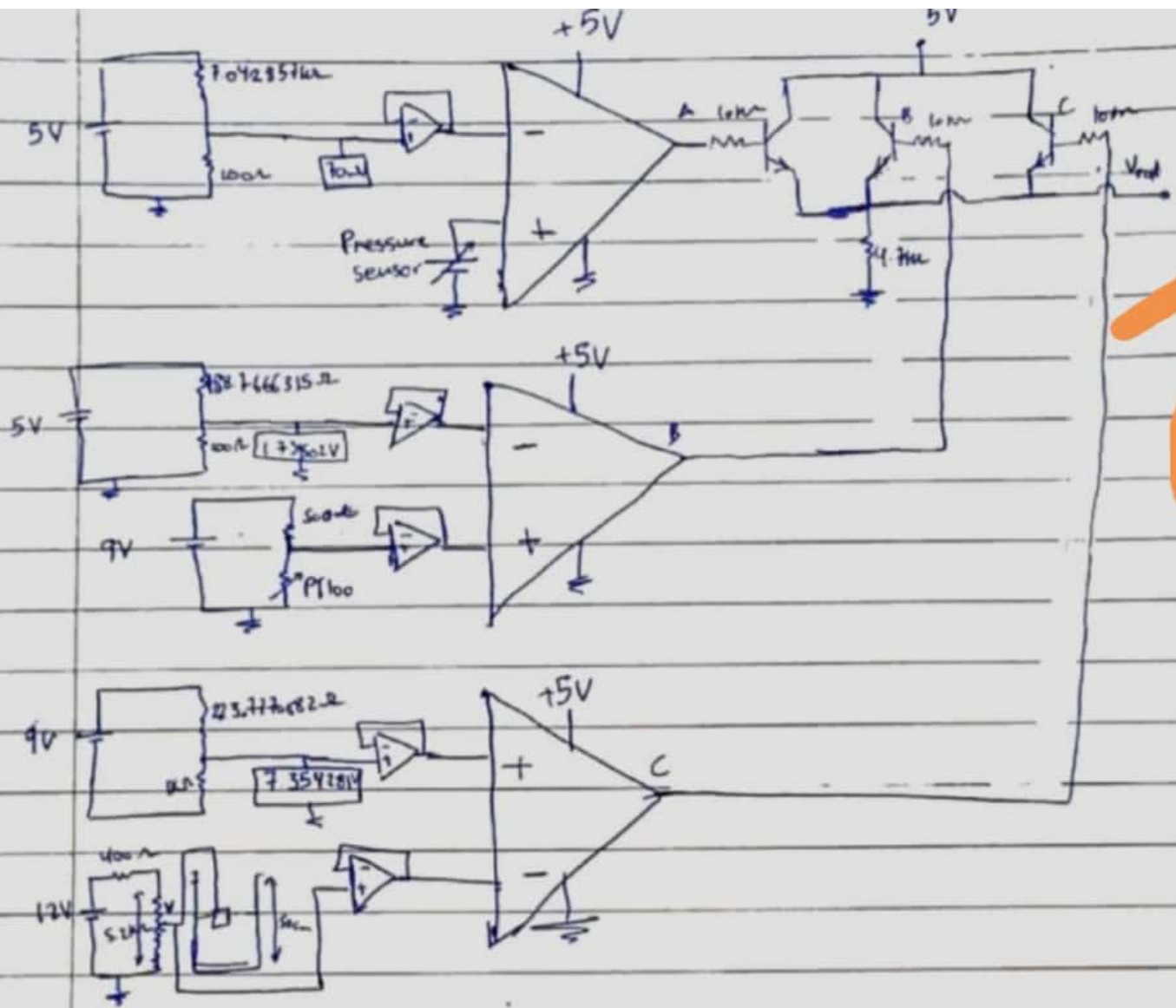
$$V = 15 \text{ bar} \times \frac{7mV}{\text{bar}} = \boxed{105mV}$$



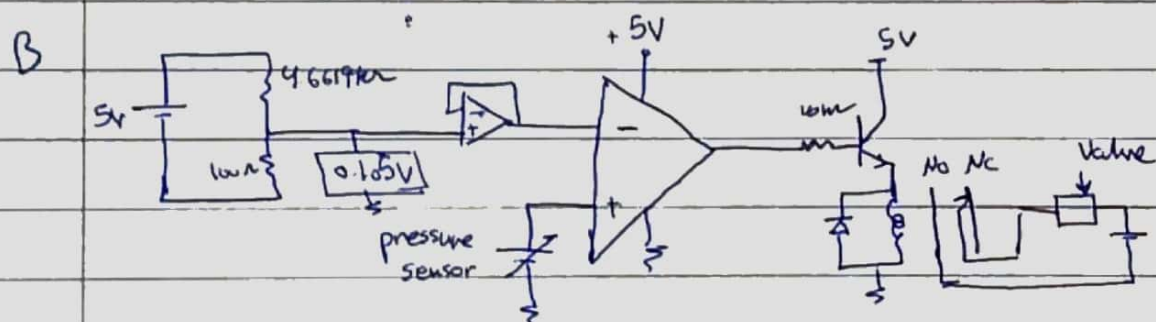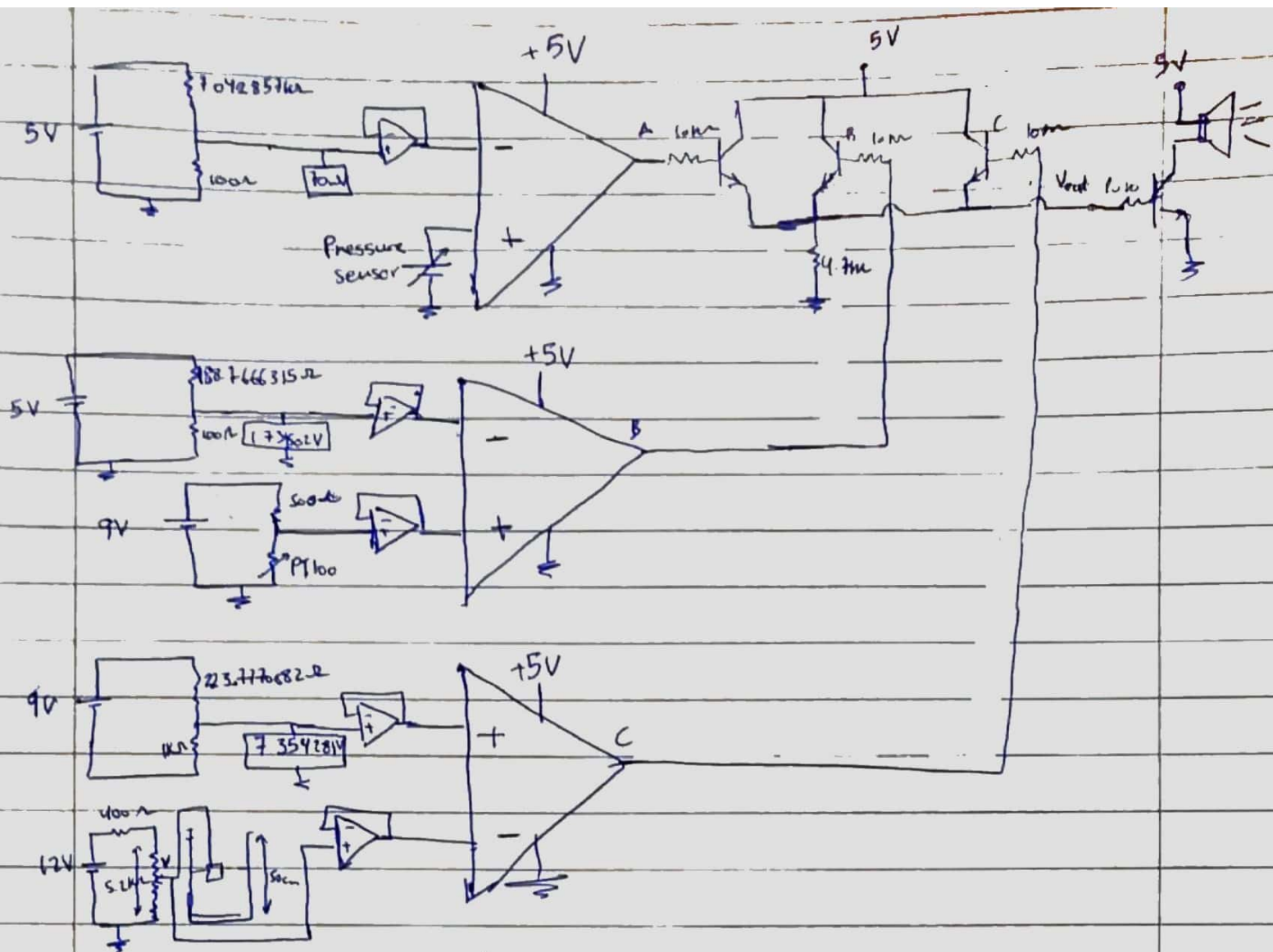

University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department

EE463


2nd Exam

Time: 1: 30 hr

spring 2018

1/1/2019

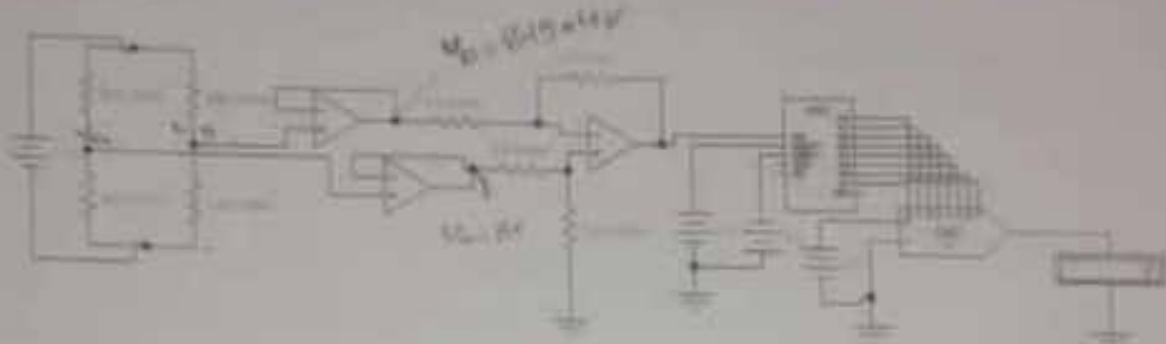Q1) From the circuit below what is the value of ADC digital outputs and DAC analog output.



Q2) A measurement signal has a frequency 800Hz, but there is unwanted noise at about 10KHz. Design filter that attenuate noise as possible with better effect on the signal (give the 3 attempts with comments).

Q3) using accelerometer which sensitivity 0.3mA/g, and using $R=200\Omega$ for voltage conversion, and using VFC which scale factor 5KHz/V, sampling time 0.1sec:

- Draw the block diagram of the operation
- What is the digital output (in binary) if the acceleration is 1.1g.
- What is the value of acceleration if the digital output is $(190)_{10}$.

Good Luck (Zeyad Hamza)

spring 2018

2nd exam

Q2

$f_s = 800 \text{ Hz}$, $f_N = 10 \text{ kHz}$

low pass filter

1) 10%

$$\frac{1}{100} = \frac{1}{\sqrt{1 + \left(\frac{10k}{f_c}\right)^2}} \rightarrow f_c = 100.005 \text{ Hz (less than } f_s)$$

for the signal

$$\frac{V_o}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{800}{100.005}\right)^2}} \times 100\% = 12.4\% \text{ very poor}$$

2) 10%

$$\frac{10}{100} = \frac{1}{\sqrt{1 + \left(\frac{10k}{f_c}\right)^2}} \rightarrow f_c = 1005037815 \text{ Hz}$$

$$\frac{V_o}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{800}{1005037815}\right)^2}} \times 100\% = 78.239693\% \text{ accepted}$$

3) 15%

$$\frac{15}{100} = \frac{1}{\sqrt{1 + \left(\frac{10k}{f_c}\right)^2}} \rightarrow f_c = 1517.165212 \text{ Hz}$$

$$\frac{V_o}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{800}{1517.165212}\right)^2}} \times 100\% = 88.4559\% \text{ better for the signal}$$

but less attenuation of noise

use 15%, take $C = 0.1 \mu\text{F}$


$$R = \frac{1}{2\pi \times 1517.165212 \times 0.1 \times 10^{-6}} \rightarrow R = 1049.028 \text{ use } R = 1k\Omega, C = 0.1 \mu\text{F}$$

$$f_c = 1591.549431 \text{ Hz}$$

$$\frac{V_o}{V_{in}} \% = 89.347637\%$$

Spring 2018 2nd

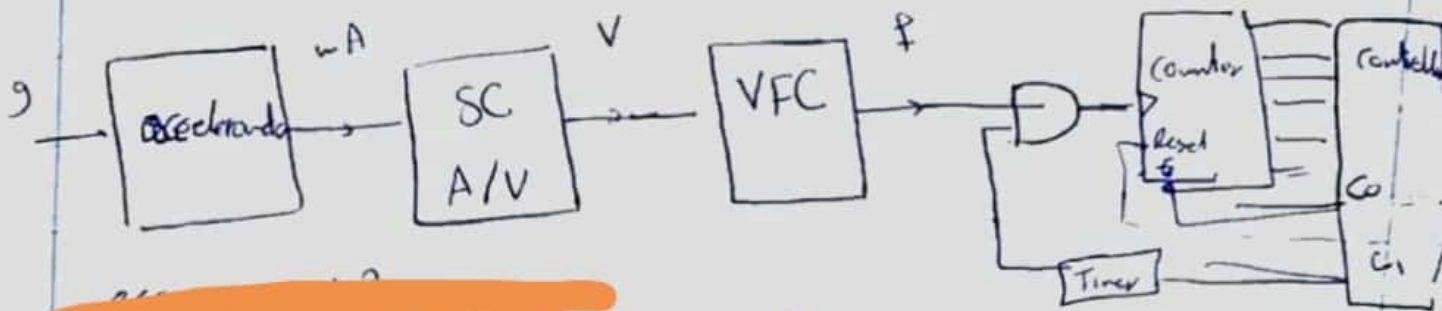Q3 $S = 0.3 \text{ mA/V}$ $R = 200 \Omega$ VFC 5 KHz/V , $T = 0.1 \text{ sec}$



SC output range $(1.2 \text{ V} \sim 1.2 \text{ V})$

VFC output range $(5 \text{ KHz} \sim 6 \text{ KHz})$

counter output range $(0 \sim 100)$

B @ $11g \rightarrow 101001010$

C if $190 \rightarrow g = 6.33$

Sample
5cc
Hz
EE463

Sample

University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department
Final Exam Time: 2 hr Spring 2018

17/7/2018

$\frac{\sqrt{KHz}}{V}$
 $\frac{1}{KHz}$

Q1) a- What is the meaning of single ended signal and differential signal. Hz

Hz
Sample
5cc
[4 pts]

b- Why sometimes we are holding the sampling signal.

Q2) Using Temperature sensor (sensitivity = 5mV/C), in the range (30C to 120C) and using voltage to frequency converter VFC (scale factor = 2V/1KHz).

$\frac{2V}{1KHz}$
 $\frac{2V}{1KHz}$

Calculate the sensor output range, and VFC output range.

Using a counter to convert to digital with sampling rate 10sample/Sec, what is the value of the output of the counter if the temperature is 112C.

75 Hz [8 pts]

Q3) Barometer sensor sensitivity is 0.13mA/bar, used for measuring pressure in the range (± 20 bar) and the value of its output @ 0 bar is 4mA, using 150 Ω , Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

$\frac{\sqrt{V}}{\sqrt{KHz}}$


a) What is the digital output of ADC at the pressure is 8 bar.

b) What is the value of pressure when the digital output is 18H.

[16 pts]

Q4) What is the value of voltmeters and ADC output.

[12 pts]

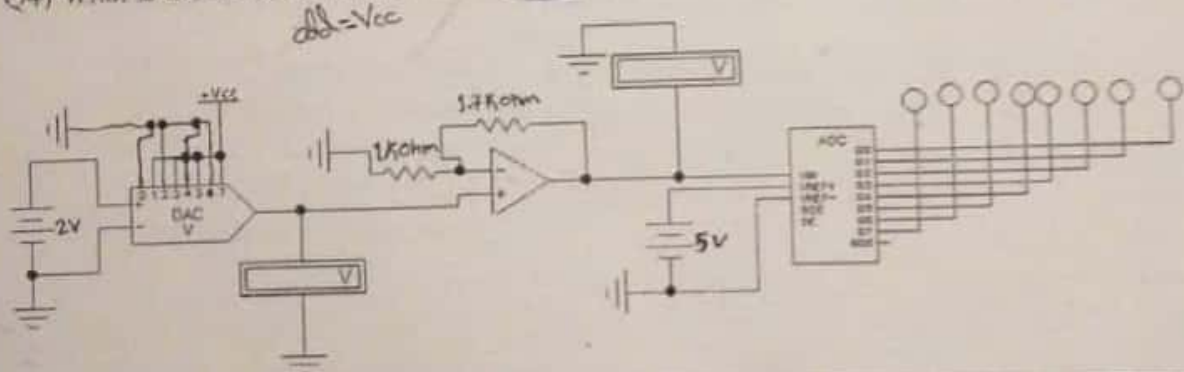

Q5) a- Using Thermocouple sensor Type J with 40C reference, What is the value of its output at the temperature 120C.

b- Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 11.4°C.

| Temperature (°C) | 0 | 5 | 10 | 15 | 20 |
|-------------------------|-------|-------|-------|-------|-------|
| Resistance (Ω) | 107.6 | 109.1 | 110.2 | 111.1 | 111.7 |

[10 pts]

Good Luck (Zeyad)

Spring 2018 final

Q2) $\dot{S} = 5 \text{ mV}/^\circ\text{C}$, $30^\circ\text{C} \sim 120^\circ\text{C}$ VFC $2\text{V}/\text{KHz}$

sensor output range ($0.15\text{V} \sim 0.6\text{V}$)

VFC sensitivity $2\text{V} \rightarrow 1\text{KHz}$
 $\dot{S} = 500\text{Hz}/\text{V}$ $1\text{V} \rightarrow ?$

VFC output range ($75\text{Hz} \sim 300\text{Hz}$)

@ 112°C $V_0 = 0.56\text{V}$, $f_0 = 280\text{Hz}$

Sampling time = 0.1sec

counter input = 28

counter output = 11100

Q3) $\dot{S} = 0.13\text{mA}/\text{bar}$ $\pm 20\text{ bar}$ @ $0\text{ bar} = 4\text{mA}$, $R = 15\text{ohm}$
 $\pm 4\text{V}$ ADC 8 b. +


sensor output range = ($1.4\text{mA} \sim 6.6\text{mA}$)

sc1 output range = ($0.21\text{V} \sim 0.99\text{V}$)

$$4 = 0.99 M + \text{offset} \quad \therefore V_{02} = 1025641 V_0 - 6153846$$

$$-4 = 0.21 M + \text{offset}$$
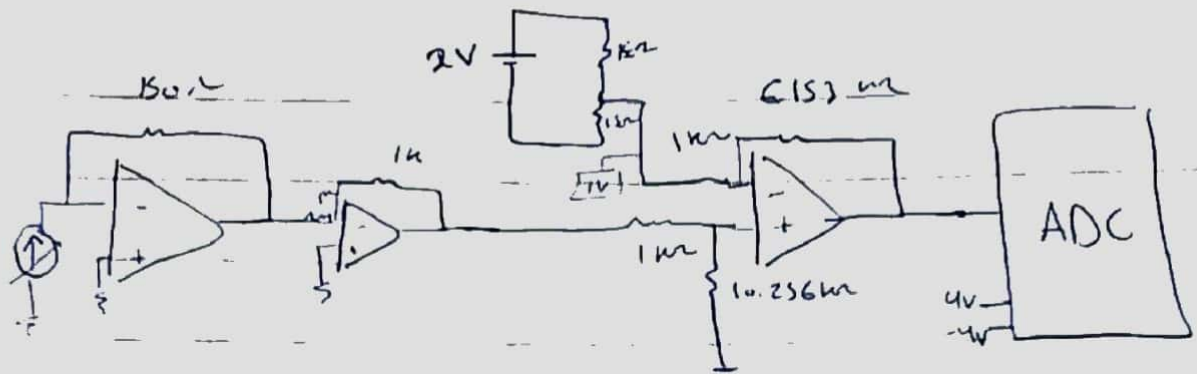
$$M = 1025641, \text{ offset} = -6153846$$



Q 8 bar $\rightarrow 1.6V$

$$\Delta V = \frac{8}{2^8} = 0.03125$$

$$\frac{1.6 + 4}{0.03125} = 179$$

$$\rightarrow \sim 179 = 10110111$$

$$18H \rightarrow (24)_{10}$$

$$V_{O2} = -3.25V$$

$$\underline{V_{O1}} = -16.25 \text{ bar}$$

Q4 $\Delta V_{DAC} = \frac{2}{2^8} = 0.0078125V$

$$\text{Digital input} = 10101010 = 170$$

$$V_1 = 1.328125V$$

$$V_2 = \left(1 + \frac{R_f}{R_i}\right) V_1 = 3.5859375V$$

$$\text{ADC } \Delta V = 0.01953125V$$

$$\text{Digital output} = 183 \rightarrow 10110111$$

$$(25a) \quad V_{J40}(120^\circ\text{C}) = V_J(120^\circ\text{C}) - V_{J0}(40^\circ\text{C})$$

$$= 6.36 \text{ mV} - 2.06 \text{ mV}$$

$$\boxed{V_{J40}(120^\circ\text{C}) = 4.3 \text{ mV}}$$

$$b) \quad R(T) = R(T_0) (1 + \alpha_1 \Delta T + \alpha_2 (\Delta T)^2)$$

$$T_1 = 0^\circ\text{C}, \quad T_0 = 10^\circ\text{C}, \quad T_2 = 20^\circ\text{C}$$

$$R(T_1) = 107.6 \Omega, \quad R(T_0) = 110.2 \Omega, \quad R(T_2) = 111.7 \Omega$$

$$R(0) = R(10) (1 + \alpha_1 (0-10) + \alpha_2 (0-10)^2)$$

$$107.6 = 110.2 (1 - 10\alpha_1 + 100\alpha_2)$$

$$0.9764065 - 1 + 10\alpha_1 - 100\alpha_2 = 0 \rightarrow \boxed{10\alpha_1 - 100\alpha_2 - 0.0235935 = 0} \rightarrow (1)$$

$$R(20) = R(10) (1 + \alpha_1 (20-10) + \alpha_2 (20-10)^2)$$

$$111.7 = 110.2 (1 + 10\alpha_1 + 100\alpha_2)$$

$$10\alpha_1 + 100\alpha_2 + 1 - 1.013612 = 0$$

$$\boxed{10\alpha_1 + 100\alpha_2 - 0.013612 = 0} \rightarrow (2)$$

$$\alpha_1 = 1.860275 \times 10^{-3}, \quad \alpha_2 = -4.99075 \times 10^{-5}$$

$$R(11.4) = R(10) (1 + \alpha_1 (11.4-10) + \alpha_2 (11.4-10)^2)$$

$$R(11.4) = 110.2 (1 + (1.860275 \times 10^{-3} \times 1.4) + (-4.99075 \times 10^{-5} \times 1.96))$$

$$\boxed{R(11.4^\circ\text{C}) = 110.4762236 \Omega}$$

Q1) a-Using RTD PT100 for temperature range (22C to 190C), design a signal conditioning circuit for (0~3V) ADC. (use voltage divider circuit, $V_s=9V$, $R_1=200\Omega$).

b-If we will send the sensor output for a distance with same voltage reference.

c-What is the ADC digital output if the temperature is 100C.

d-What is the temperature if the ADC output is (10011110).

$V_{red} = 2V$ [14 pts]

Q2) Using Acceleration sensor (sensitivity = $0.14mA/g$), with offset $7mA@0g$, for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor = $4V/6KHz$).

a-Draw the block diagram of the operation.

b-Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.


c-What is the value of the output of the counter if the acceleration is $-0.5g$. [10 pts]

Q3) Barometer sensor sensitivity is $5mV/bar$, and $5\Omega/cm$ pot. level sensor for 150cm range used for measuring level ($V_s=9V$ use, $R_1=150\Omega$), Design circuit to turn ON green LED if (level more than 70cm and pressure less than 5bar), red LED if one of them opposite these values.

[10 pts]

Q4) What is the value of voltmeters and ADC and DAC outputs.

[8 pts]

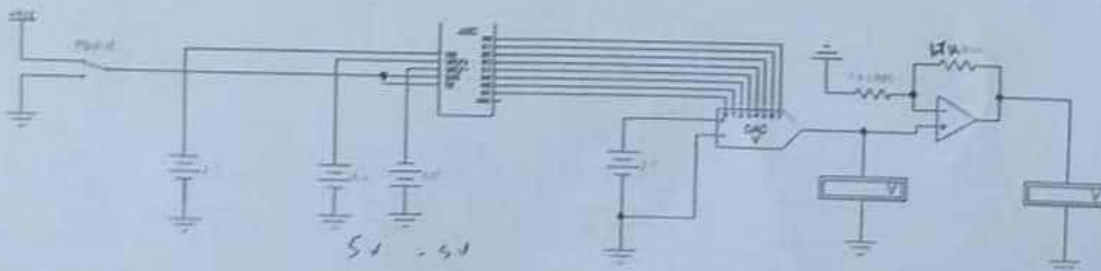

Q5) a- Using Thermocouple sensor Type K with 0C reference, What is the value of temperature if its output is 19mV, What is its output at the temperature $V_{K10}(-40C)=?$. [8pts]

Good Luck (Zeyad)

Fall 2018 Final

Q1) PT100 ($22^{\circ}\text{C} \sim 190^{\circ}\text{C}$) ADC $0 \sim 3\text{V}$

$V_s = 9\text{V}$, $R_i = 200\Omega$

sensor output range = ($108.58\Omega \sim 174.1\Omega$)


VD output range = ($3.166829\text{V} \sim 4.188452\text{V}$)

$3 = 4.188452\text{M}$, offset

$0 = 3.166829\text{M}$, offset

$M = 2.936504$, offset = -9.299406
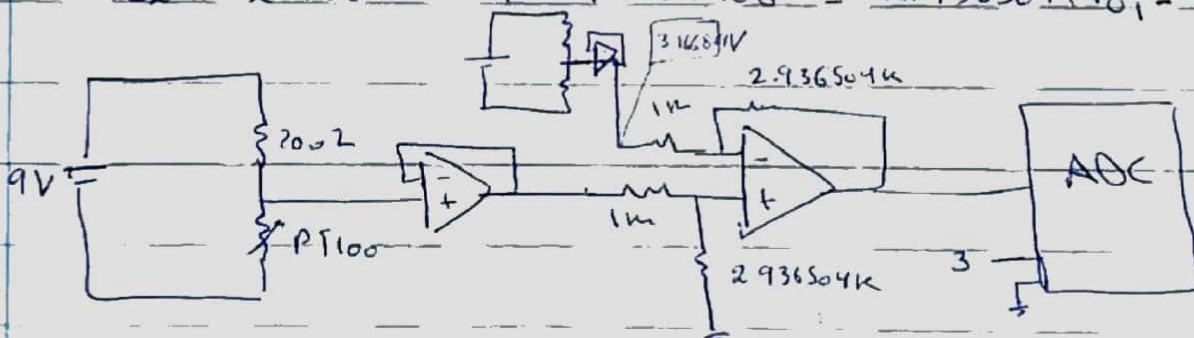
$$V_{O2} = 2.936504 V_{O1} - 9.299406 = 2.936504 (V_{O1} - 3.166829)$$



$$\Delta V = \frac{3}{2^8} = 0.01171875\text{V}$$


@ 100°C $V_{O2} = 1.537073 \rightarrow \text{Digital output} = 131 = 10000011$

@ $10011110 \rightarrow 158 \rightarrow V_{O2} = 0.9140625 = 1.8515625$

$V_{O1} = R = 115.975 \quad T = 117.8931^{\circ}\text{C}$

$\rightarrow T = 66.6026^{\circ}\text{C}$

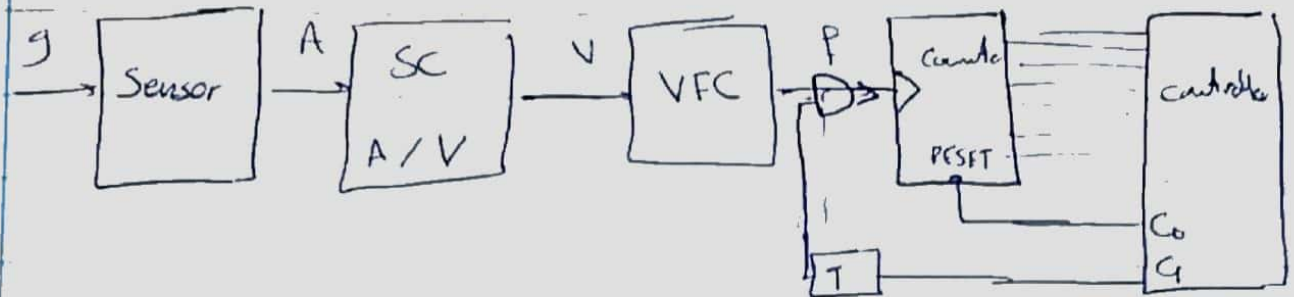Q2) $\dot{F} = 0.14 \text{ mA/g}$ @ $\theta_g = 7 \text{ mA}$ $\pm 30 \text{ g}$ VFC
 4 V/6 kHz



Sensor output range = $(2.8 \text{ mA} \sim 11.2 \text{ mA})$

use $R = 500 \Omega$

Voltage output range = $(1.4 \text{ V} \sim 5.6 \text{ V})$

VFC $\rightarrow 4 \text{ V} \rightarrow 6 \text{ kHz}$

$1 \text{ V} \rightarrow x$

$$\frac{6 \text{ kHz} \times 1 \text{ V}}{4 \text{ V}} =$$

VFC $\rightarrow 1.5 \text{ kHz/V}$

VFC output range $(2.1 \text{ kHz} \sim 8.4 \text{ kHz})$

counter output $(420 \sim 1680)$

c. @ $-0.5 \text{ g} \rightarrow 1039.5 \approx 1039$

Q3). $p^+ = 5 \text{ mV/bar}$, $5 \Omega / \text{cm}^2$ ~~per~~ 15 cm , $V_s = 9 \text{ V}$, $R = 150 \Omega$

at 70 cm


$$R = \frac{5 \Omega}{\text{cm}} \times 70 \text{ cm} = 350 \Omega$$

at 150 cm $\rightarrow R_{\text{tot}} = \frac{5 \Omega}{\text{cm}} \times 150 \text{ cm} = 750 \Omega$

$$V = 9 \times \frac{350}{750 + 150} = \boxed{3.5V}$$

at 5 bar

$$V = 25 \text{ mV}$$

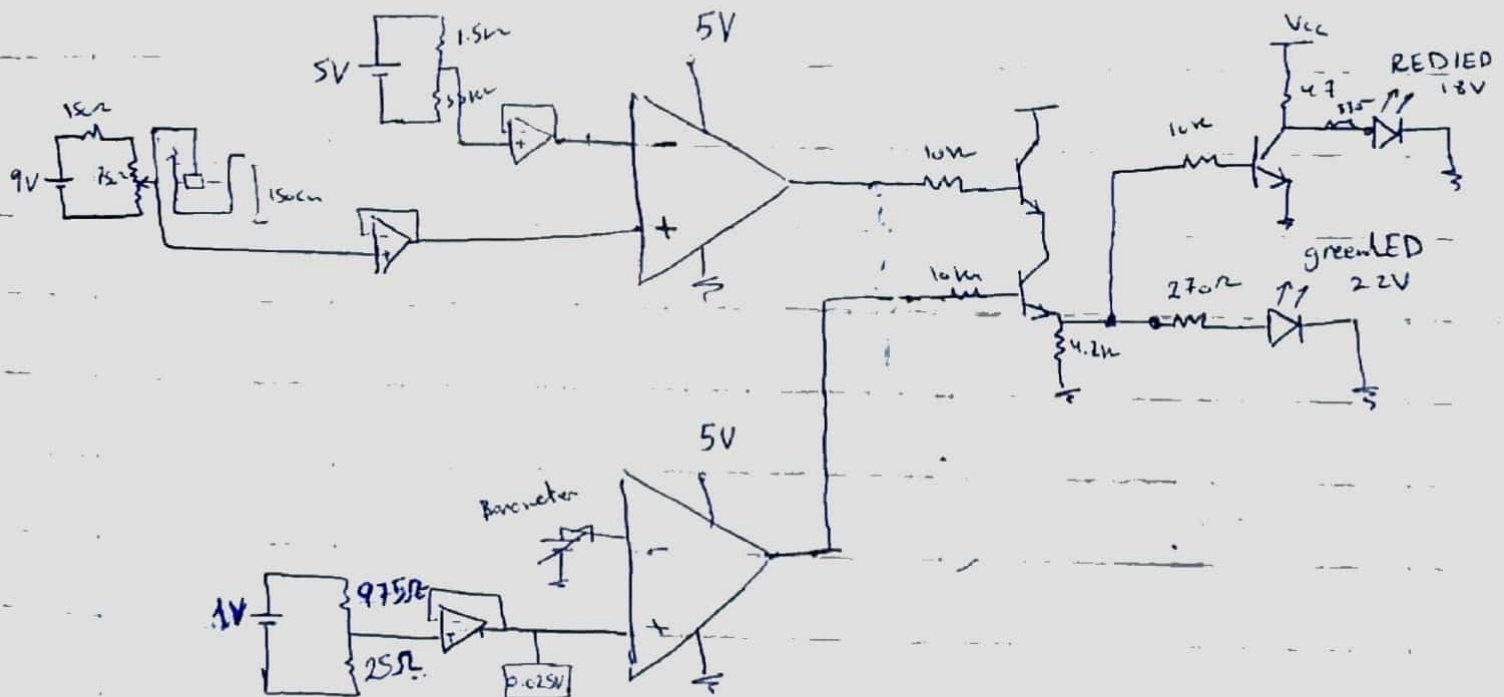

Q5 $V_M = 19 \text{ mV}$, 0°C reference

T V

L 460 18.94 mV

M T_M 19 mV

H 465 19.15 mV

$$T_M = T_L + \frac{T_H - T_L}{V_H - V_L} (V_M - V_L)$$

$$= 460 + \frac{465 - 460}{19.15 - 18.94} (19 - 18.94)$$

$$T_M = 461.4285714^\circ\text{C}$$

b) $V_{k10}(-40^\circ\text{C}) = V_{k0}(-40^\circ) - V_{k0}(10^\circ)$
 $= -1.5 - 0.4$

$$V_{k10}(-40^\circ\text{C}) = -1.9 \text{ mV}$$

Q1) a- What is the meaning of single ended signal, differential signal and give example.

b- What is sample and what is hold and when we use them.

[6 pts]

Q2) Using Temperature sensor (RTD-PT100), in the range (30°C to 90°C) and using Wheatstone bridge ($V_s=9V$, $R_1=110$, $R_2=120$), and using voltage to frequency converter VFC (scale factor = $10\text{KHz}/1.12V$).

a- Calculate the sensor output range, Wheatstone bridge output range and VFC output range.

b- Using a counter to convert to digital with sampling rate 180 sample/Sec, What is the output range of the counter, what is the value of the output of the counter if the temperature is ~~100°C~~ 55°C .

c- Draw Block diagram of the circuit.

[16 pts]

Q3) An accelerometer sensor sensitivity is 0.145mA/g , used for measuring pressure in the range ($\pm 20\text{g}$). and the value of its output @ 0g is 5.2mA , using 190Ω converting to volt resistance, Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

a) Calculate sensor output range (current, voltage, Binary).

$$= \frac{I_{\text{out}} + V_{\text{ref}}}{R_V}$$

b) What is the digital output of ADC at the acceleration is 8g .

c) What is the value of acceleration when the digital output is $0DH, 92H$. [15 pts]

d) If the frequency of the signal is 120Hz and there is unwanted noise with frequency 15KHz , design filter that attenuate the noise to 18% of its value, calculate the effect on the sensor output range. [05 pts]

Q4) Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 12.4°C .

| Temperature ($^\circ\text{C}$) | 0 | 5 | 10 | 15 | 20 |
|----------------------------------|-------|-------|-------|-------|-------|
| Resistance (Ω) | 103.6 | 105.1 | 106.3 | 107.1 | 108.3 |

190

103.6

105.1

106.3

107.1

108.3

[08 pts]



Good Luck (Zeyad)

spring 2019

Q2) PT100 (30°C ~ 90°C) $V_s = 9$, $R_1 = 110\Omega$, $R_2 = 120\Omega$
VFC 10 kHz / 1.12V

a) sensor output range (111.7 Ω ~ 135.1 Ω)

for bridge $R_2 R_3 = R_1 R_4 \rightarrow R_3 = \frac{R_1 R_4}{R_2}$

$$R_4 = 111.7\Omega \rightarrow R_3 = 102.3916667\Omega$$

$$\text{at } 30^\circ\text{C} \quad V_A = 9 \times \frac{111.7}{111.7 + 120} = 4.3388002\text{V}$$

$$V_B = 9 \times \frac{102.3916667}{102.3916667 + 110} = 4.3388002\text{V}$$

$$V_0 = V_A - V_B = 0$$

$$\text{at } 90^\circ\text{C} \quad V_A = 9 \times \frac{135.1}{135.1 + 120} = 4.766366\text{V}$$

$$V_B = 4.3388002 \rightarrow V_0 = V_A - V_B \rightarrow V_0 = 0.427564\text{V}$$

bridge output range (0V ~ 0.427564V)

$$\text{VFC} \quad 10\text{kHz} \quad 1.12\text{V} \rightarrow = \boxed{8.928571\text{kHz/V}}$$

2 1V

VFC output range (0 ~ 3.817536 kHz)


$$\frac{180 \text{ sample}}{\text{sec}} \rightarrow T = 0.005556 \text{ sec}$$

Counter output range (0 ~ 21.21023)


(0 ~ 21)

(00000 ~ 10101)

@ 55°C → 01001

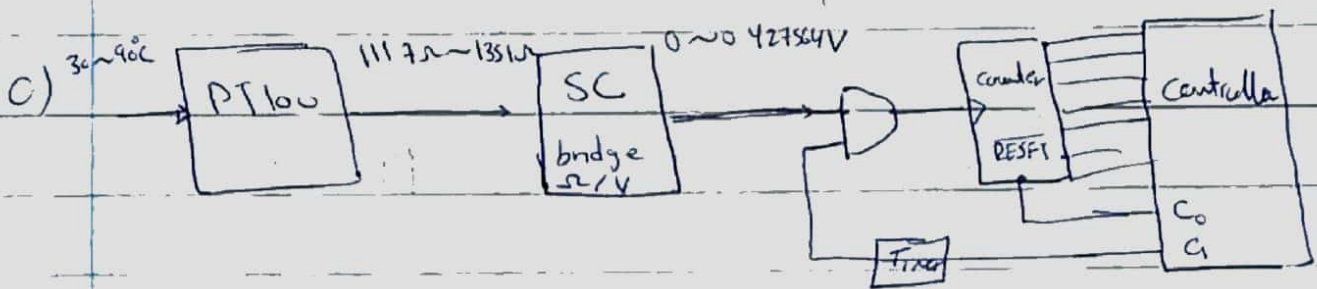

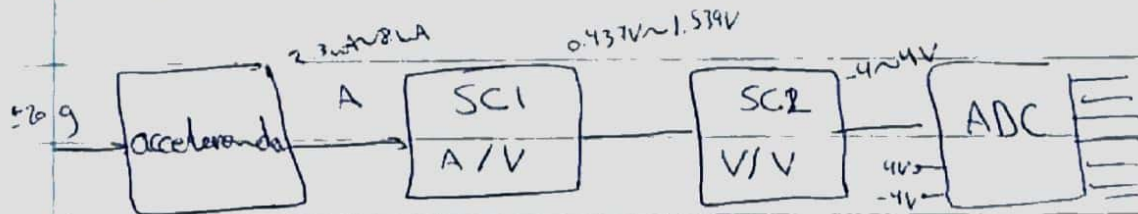Q3) 0.145mA/g ± 20g @ 0g = 5.2mA, R = 180Ω
ADC +4V



sensor output range (2.3mA ~ 8.1mA)

SCI voltage range (0.437V ~ 1.539V)

$$4 = 1.539M + \text{offset}$$

$$-4 = 0.437M + \text{offset}$$

$$V_2 = 7.259528V_1 - 7.172414$$

$$M = 7.259528, \text{offset} = -7.172414$$

Binary range (00000000 ~ 11111111)

b @ 8g $V_{02} = 1.5999996V$

$$\Delta V = \frac{8}{2^8} = 0.03125$$

~~Digital~~ output = 51 = ~~00110011~~

Digital output = 179 = 10110011

c 0D \rightarrow 13 $\rightarrow V_{02} = -3.59375, -17.968749g$
92 \rightarrow 146 $\rightarrow V_{02} = \rightarrow$ ~~13.125g~~ 2.8125g

$$Q4) R(T) = R(T_0) \{ 1 + \alpha_1 \Delta T + \alpha_2 (\Delta T)^2 \}$$

$$T_0 = 0^\circ\text{C} \rightarrow R(0) = 103.6 \Omega$$

$$T_0 = 10^\circ\text{C} \rightarrow R(10) = 106.3 \Omega$$

$$T_2 = 20^\circ\text{C} \rightarrow R(20) = 108.3 \Omega$$

$$R(0) = R(10) (1 + \alpha_1 (0-10) + \alpha_2 (0-10)^2)$$

$$103.6 = 106.3 (1 - 10\alpha_1 + 100\alpha_2)$$

$$10\alpha_1 - 100\alpha_2 - 0.0253998 = 0 \rightarrow (1)$$

$$R(20) = R(10) (1 + \alpha_1 (20-10) + \alpha_2 (20-10)^2)$$

$$108.3 = 106.3 (1 + 10\alpha_1 + 100\alpha_2)$$

$$10\alpha_1 + 100\alpha_2 - 0.0188147 = 0 \rightarrow (2)$$


$$\alpha_1 = 2.210725 \times 10^{-3}, \alpha_2 = -3.29255 \times 10^{-5}$$

$$R(12.4) = R(10) (1 + \alpha_1 (12.4-10) + \alpha_2 (12.4-10)^2)$$

$$R(12.4) = 106.3 (1 + (2.210725 \times 10^{-3} \times 2.4) - (3.29255 \times 10^{-5} \times 5.76))$$

$$R(12.4) = 106.8438403 \Omega$$

Q1) Using Temperature sensor PT200 with (sensitivity = $0.39/^{\circ}\text{C}$), in the range (-15°C to 180°C) in voltage divider which $V_s=12\text{V}$, $R_1=180\Omega$, and use voltage to frequency converter VFC (scale factor = $5\text{KHz}/1.2\text{V}$) and counter to convert the signal to digital form (Sampling rate : 20 sample/Sec)

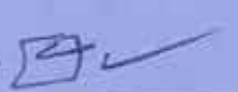- Draw Block diagram of the circuit.
- Calculate the sensor output range, voltage divider, VFC, counter output range.
- What is counter output if the temperature is 112°C .
- What is the temperature if digital output is $(1111101000)_2$. 

Q2) An accelerometer sensor sensitivity is 0.1mA/g , used for measuring pressure in the range ($\pm 20\text{g}$). and the value of its output @ $0\text{g} = 1.2\text{mA}$, using 140Ω converting to volt resistance, send signal long distance and design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 3\text{V}$.

- Draw block diagram, and circuit diagram.
- Calculate sensor output range, (I/V) range?
- What is the digital output of ADC at the acceleration is 11g .
- What is the value of acceleration when the digital output is $(1000000)_2$.



3) Using the accelerometer MS1010 which its sensitivity = 270mv/g , range $\pm 10\text{g}$, and sampling rate is 5 sample/sec. Complete the following table.

| Time(mS) | Acc. Output (mv) | Acc. (g) | Acc. (m/s^2) | Velocity (m/s) | Displacement (m) |
|----------|------------------|----------|-------------------------|---------------------------|------------------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 200 | 420 | | | | |
| 400 | 970 | | | | |
| 600 | 1500 | | | | |

$$v(t) \text{ m/s} = v(t-1) + \left(a(t) + a(t-1) \right) \frac{T}{2}$$

$$pos[t] \text{ m} = pos[t-1] + \left(v(t) + v(t-1) \right) \frac{T}{2}$$


Good Luck (Eng. Zeyad Shennib)

~~Exam~~

Fall 2019

Midterm

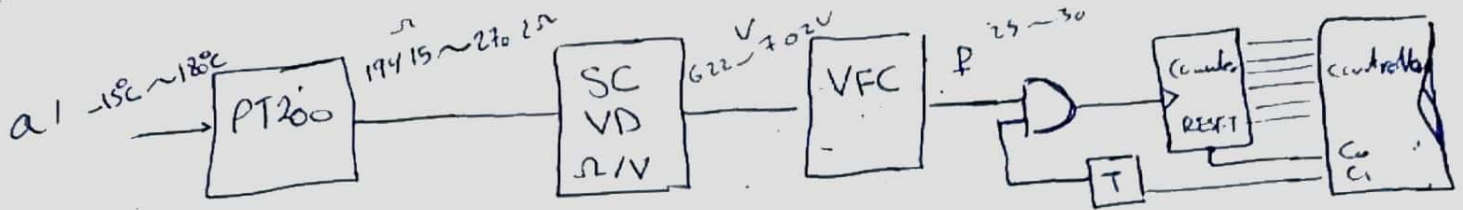Q1) PT200, $0.39 \Omega/^\circ\text{C}$ ($-15^\circ\text{C} \sim 180^\circ\text{C}$) $V_D V_S = 12\text{V}$
 $R_1 = 180 \Omega$ VFC $5\text{KHz}/1.2\text{V}$, sampling rate 20 sample/sec



b) sensor range ($-15^\circ\text{C} \sim 180^\circ\text{C}$)
 sensor output range $(-15^\circ\text{C} \times 0.39 \frac{\Omega}{^\circ\text{C}}) + 200 \Omega \sim (180^\circ\text{C} \times 0.39 \frac{\Omega}{^\circ\text{C}}) + 200 \Omega$
 ($194.15 \Omega \sim 270.2 \Omega$)

voltage divider output range $(12 \times \frac{194.15}{194.15 + 180}) \sim (12 \times \frac{270.2}{270.2 + 180})$

$= (6.226914\text{V} \sim 7.202132\text{V})$

VFC $5\text{KHz} \rightarrow 1.2\text{V} \rightarrow 4.166667 \text{ KHz/Vol}$

$\times \rightarrow 1\text{V}$

VFC output range = ($25.945477 \text{ KHz} \sim 30.008885 \text{ KHz}$)

sampling time = 0.05 sec

counter output range = ($1297 \sim 1500$)

$= (10100010001 \sim 1011011100)$

c) @ $112^{\circ}\text{C} \rightarrow \text{sensor output RTD} = 112 \times 0.391 + 200$
 $= 243.68 \Omega$

$$V_{\text{RTD}} = 12 \times \frac{243.68}{243.68 + 180} = 6.901813 \text{ V}$$

$$f = 28757556 \text{ KHz}$$


$$\text{counter output} = 1437$$

$$= 10110011101$$

d) $(1000)_{10}$ counter output $A = 1000$ out of range

$$f = \frac{1000}{0.05} = 20 \text{ KHz}$$

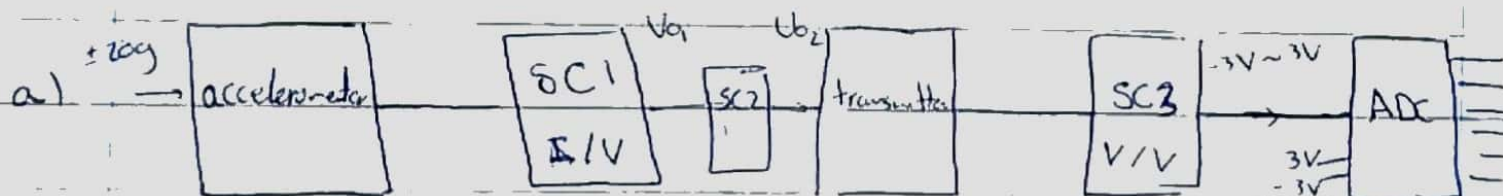Q2 $S = 0.1 \text{ mA/g}$, $\pm 20 \text{ g}$ @ $I_0 = 1.2 \text{ mA}$, $R = 140 \Omega$
 long distance ADC 8-bit $\pm 3 \text{ V}$



sensor output range $(\pm 20 \text{ g} \times 0.1) + 1.2 \sim (20 \times 0.1) + 1.2$
 $= (-0.8 \text{ mA} \sim 3.2 \text{ mA})$

SC1 I/V output range $= (-0.8 \times 14 \sim 3.2 \times 14)$
 $= (-0.112 \text{ V} \sim 0.448 \text{ V})$

SC2 $\rightarrow V_{02} = V_{01} + 2 \rightarrow \text{range } (1.888 \text{ V} \sim 2.448 \text{ V})$

for SC3


$$3 = 2.448 \text{ M} + \text{offset}$$

$$\underline{-3 = 1.888 \text{ M} + \text{offset}}$$

$$M = 10.714286, \text{ offset} = -23.228572$$

$$V_{O3} = 10.714286 V_{O2} - 23.228572$$

$$V_{O3} = 10.714286 (V_{O2} - 2.168)$$

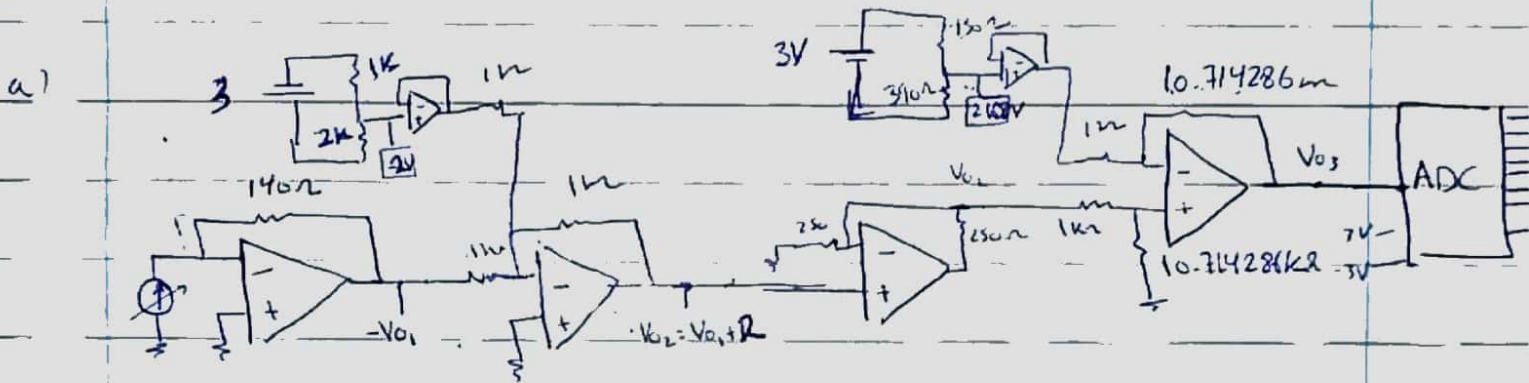

c) $11g \rightarrow I = 2.3 \text{ mA} \quad \Delta V = \frac{6}{2^8} = 0.0234375$

$$V_{O1} = 0.322 \text{ V}$$

$$V_{O2} = 2.322 \text{ V}$$

$$V_{O3} = 1.65 \text{ V}$$

$$\text{Digital output} = \frac{1.65 + 3}{0.0234375} = 198$$

$$= 11000110$$

d) 0010 0000 \rightarrow 32

$$V_{03} = -2.25V$$

$$V_{02} = 1.958V$$

$$V_{01} = -0.042V$$

$$I = -0.3\mu A$$

$$\text{acceleration} = -15g$$

Q3)

| T | acc (mV) | acc (g) | acc (m/s ²) | Velocity (m/s) | Displacement (m) |
|-----|----------|----------|-------------------------|----------------|------------------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 200 | 420 | 1.555556 | 15.260004 | 1.5260004 | 0.15260004 |
| 400 | 970 | 3.592593 | 35.243337 | 6.5763345 | 0.862834 |
| 600 | 1500 | 5.555556 | 54.500004 | 15.556686 | 3.175534 |


$$V(t) = V(t-1) + \frac{T}{2} [A(t) + A(t-1)]$$

$$\text{pos}(t) = \text{pos}(t-1) + \frac{T}{2} [V(t) + V(t-1)]$$

Q1) In climatic test room using T-type thermocouple sensor and using the following signal conditioning circuit, Calculate: a- The digital output if the temperature is 25F.

b- What is the temperature ($^{\circ}\text{C}$) if the digital output is (10001011).

[18 pts]

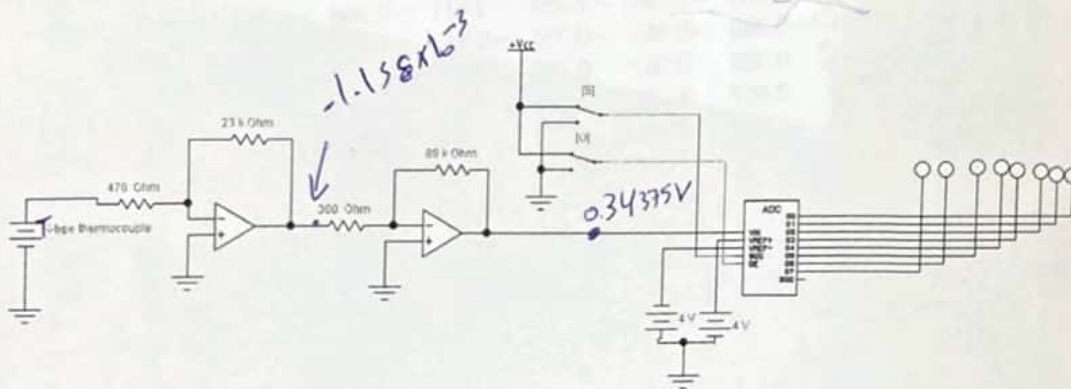

Q2) Using RTD type (PT200) in the temperature range (-20°C to 120°C), as a resistance R_4 in Wheatstone bridge, $R_1=190\Omega$, $R_2=215\Omega$, $V_s=12\text{V}$.

a- Calculate sensor output range, calculate R_3 for balancing the bridge?, calculate the bridge output voltage range? 169.85

b- Using VFC (5.4Khz/2.5V) for A/D conversion, calculate VFC output range?

c- What is the counter output range with sampling rate 12sample/sec? and what is counter output if temperature is -5°C ? 16.164

d- Draw Block diagram of the circuit.

[18 pts]

Q3) An accelerometer, with sensitivity is 0.95mA/g , used for measuring acceleration in the range ($\pm 15\text{g}$) and the value of its output @ 0g is 3.6mA , using 150Ω converting to volt resistance, Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 5\text{V}$.

a) Calculate sensor output range (current, voltage). 1.36

b) What is the digital output of ADC at the acceleration is 1g ? 1.87

c) What is the value of acceleration when the digital output is 09H, 90H? -13.94

[16 pts]

Q4) Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 7°C . Is the sensor PTC or NTC and why?

| | | | | | |
|------------------------------------|-------|-------|-------|-------|-------|
| Temperature ($^{\circ}\text{C}$) | 0 | 4 | 8 | 12 | 16 |
| Resistance (Ω) | 102.6 | 104.1 | 105.3 | 106.1 | 107.3 |

[08 pts]

Good Luck (Zeyad)

Final Exam

Fall 2019

Q1)

$$25F = \frac{5}{9}(25-32) = -3.888889^{\circ}C$$

| | T | V | |
|---|-----------|--------|---|
| L | -5 | -0.191 | $V_M = V_L + \frac{V_H - V_L}{T_H - T_L} (T_M - T_L)$ |
| M | -3.888889 | V_M | |
| H | -0 | -0 | $V_M = -0.191 + \frac{-0 - (-0.191)}{-0 - (-5)} (-3.888889 - (-5))$ |

$$V_M = -0.148556mV$$

after inverting amp $V_2 = -\frac{23k\Omega}{470\Omega} \times -0.148556$

$$V_2 = 7.269762mV$$

$$V_3 = -\frac{89k\Omega}{300\Omega} \times 7.269762$$

$$V_3 = -2.156696V$$

for the ADC $\Delta V = \frac{4 - (-4)}{2^8} = 0.03125mV$

$$\text{Digital output} = \frac{-2.156696 + 4}{0.03125} = \boxed{59 - 00111011}$$

b' $10001011 \rightarrow 139$ $139 = \frac{V_3 + 4}{0.03125} \rightarrow V_3 = 0.34375V$

$$V_3 = -\frac{89k\Omega}{300\Omega} V_2 \rightarrow V_2 = -1.158708mV$$

$$V_2 = -\frac{23k\Omega}{470\Omega} V_1 \rightarrow V_1 = 0.02367794mV$$


| | T | V |
|---|-------|------------|
| L | 0 | 0 |
| M | T_M | 0.02367794 |
| N | 5 | 0.193 |

$$T_M = T_L + \frac{T_M - T_L}{V_M - V_L} (V_M - V_L)$$

$$T_M = 0 + \frac{5 - 0}{0.193 - 0} (0.02367794 - 0)$$

$$T_M = 0.613418^\circ\text{C} \quad T = 33.10415^\circ\text{F}$$

Q2

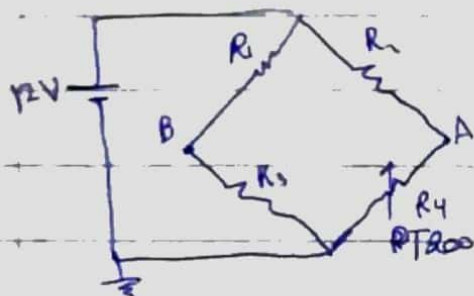

For PT200 $(-20^\circ\text{C} \sim 120^\circ\text{C})$

$$\text{sensor output range} = (-20^\circ\text{C} \times 3.92 + 20^\circ\text{C} \times 120.5) \sim 246.8\Omega$$

$$= (192.2\Omega \sim 246.8\Omega)$$

For balance $\frac{R_1}{R_3} = \frac{R_2}{R_4}$, $R_3 = \frac{R_1 R_4}{R_2}$

$$R_3 = \frac{190 \times 192.2}{215} = 169.8511628\Omega$$

voltage output range: @ -20°C

$$V_A = \frac{12 \times 192.2}{192.2 + 215} = 5.664047\text{V}$$

$$V_B = 12 \times \frac{169.8511628}{169.85} = 5.664047\text{V}$$

$$V_A = V_B \rightarrow \Delta V = 0\text{V}, \text{ @ } 120^\circ\text{C}$$

$$V_A = 12 \times \frac{246.8}{246.8 + 215} = 6.413166\text{V}, V_B = 5.664047$$

$$\Delta V = V_A - V_B = 0.749118\text{V}$$

voltage output range = $(0 \sim 0.749118\text{V})$

b) $\frac{5.4 \text{ kHz}}{2.5 \text{ V}} = 2.16 \text{ kHz/V}$

VFC output range = (0 ~ 1618095 kHz)

c) $T = \frac{1}{12} = 0.0833333$

counter output range = (0 ~ 134) ~~(0000000000000000)~~


if $T = -5^\circ\text{C} \rightarrow R_4 = 1510.39 + 200 = 198.05 \Omega$

$V_a = 12 \times \frac{198.05}{198.05 + 215} = 5.753783 \text{ V}, V_b = 5.664077$

$V_d = 0.089736$


$f = 0.19382976 \text{ kHz}$

counter output = 16 = (00010000)

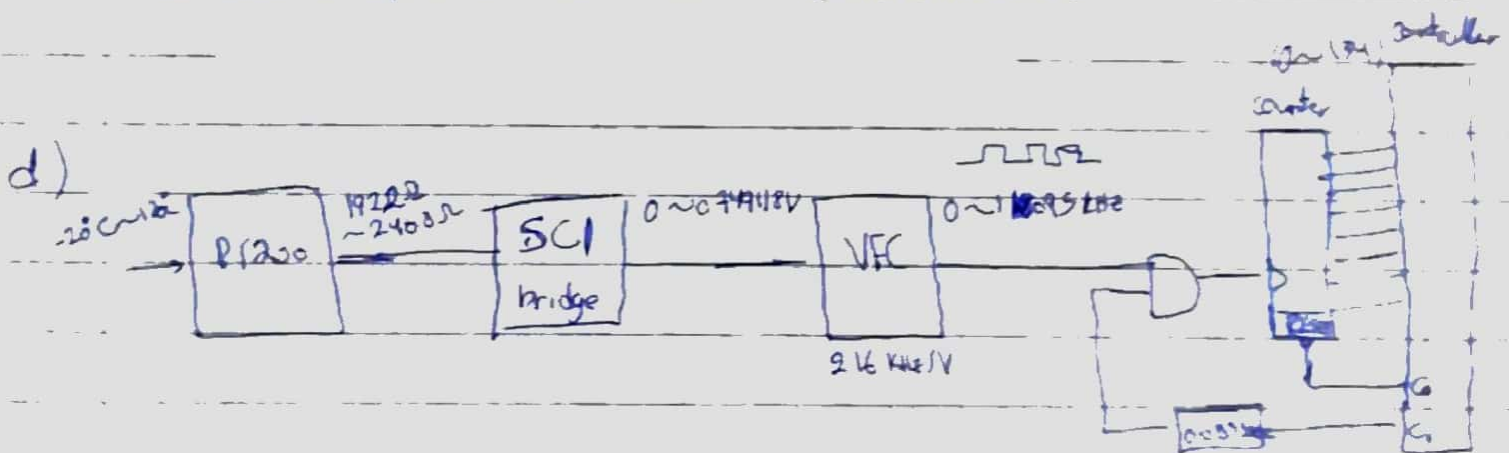

Q3 Accelerometer current output range $= (-15 \times 0.45) + 3.6 \sim (15 \times 0.45) + 3.6$
 $= (-10.65 \text{mA} \sim 17.85 \text{mA})$

Voltage output range $= (-1.5975 \text{V} \sim 2.6775 \text{V})$

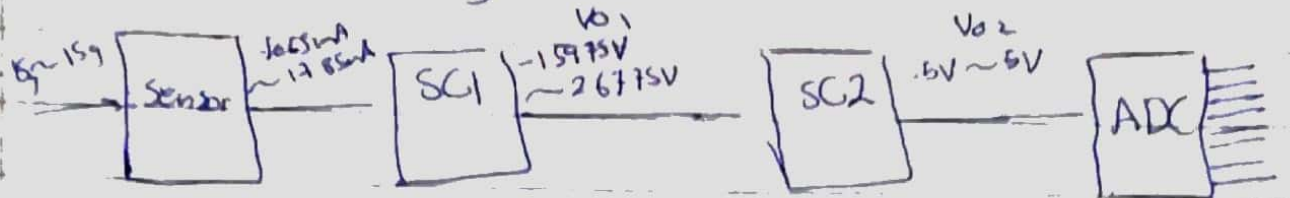

SC2

$$5 = 2.6775 M + \text{offset}$$


$$-5 = -1.5975 M + \text{offset}$$

$$M = 2.3391813, \text{ offset} = -1.263158$$

$$V_o = 2.3391813 V_{in} - 1.263158$$

| | | | |
|-----------|------------|-----------------------|------------|
| V_{in} | -1.5975 | 0.54 | 2.6775 |
| V_{out} | -5.0000001 | -9.8×10^{-8} | 4.99999993 |

محول التحويل

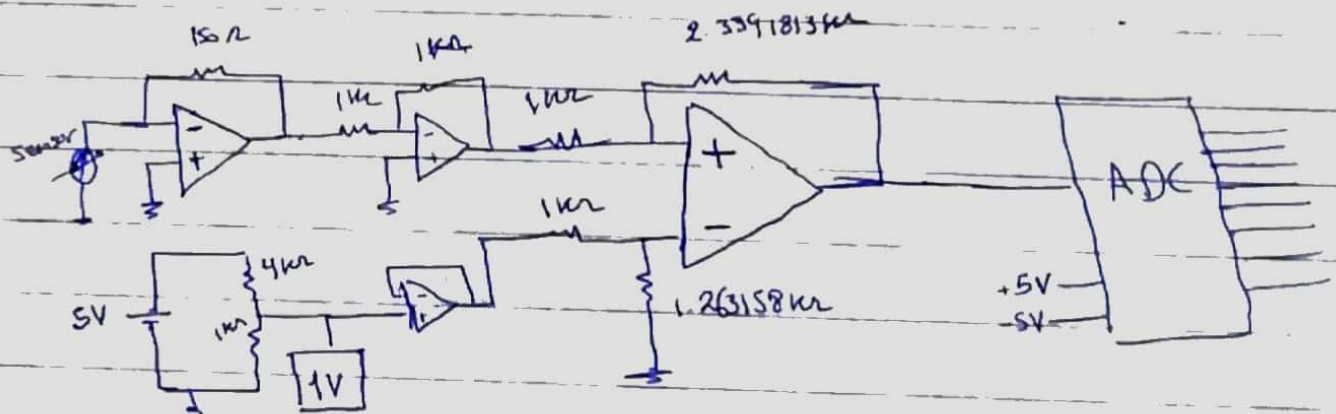

b) @ 1g $\rightarrow I = 4.55 \mu A$

$V_0 = 0.6825 V$

$V_{02} = 0.3333332 V$

For the ADC $\Delta V = \frac{5 - (-5)}{2^8} = 0.0390625 V$

Digital output = $\frac{0.3333332 + 5}{0.0390625} = 136 = 10001000$

P

c) 09H $\rightarrow 1001$
 $= 9$

90H $\rightarrow 10010000$
 $= 144$

$9 = \frac{V_{02} + 5}{\Delta V} \rightarrow \frac{V_{02} + 5}{0.0390625} = 9$

$144 = \frac{V_{02} + 5}{\Delta V}$

$V_{02} = -4.6484375 V$

$V_{02} = 0.625 V$

$V_{02} = 2.391813 V_{01} - 1.263158$

$V_{01} = 0.8071875 V$

$V_{01} = -1.447207 V$

$I = 5.3812503 \mu A$

$I = \frac{V_{01}}{R} = -9.6480467 \mu A$

$a = 1.875 g$

$I = (a \times 0.95) + 3.6$

$a = -13.945312 g$

$$R(T) = R(T_0) (1 + \alpha_1 \Delta T + \alpha_2 (\Delta T)^2)$$

$$T_1 = 0^\circ \rightarrow R(0) = 102.6 \Omega$$

$$T_0 = 8^\circ \rightarrow R(8) = 105.3 \Omega$$

$$T_2 = 16^\circ \rightarrow R(16) = 107.3 \Omega$$

$$R(0) = R(8) (1 + \alpha_1 (0-8) + \alpha_2 (0-8)^2)$$

$$102.6 = 105.3 (1 - 8\alpha_1 + 64\alpha_2)$$

$$8\alpha_1 - 64\alpha_2 - 0.02564103 = 0 \rightarrow (1)$$

$$R(16) = R(8) (1 + \alpha_1 (16-8) + \alpha_2 (16-8)^2)$$

$$107.3 = 105.3 (1 + 8\alpha_1 + 64\alpha_2)$$

$$8\alpha_1 + 64\alpha_2 - 0.01899335 = 0 \rightarrow (2)$$

$$\alpha_1 = 2.78964875 \times 10^{-3}, \quad \alpha_2 = -5.1935 \times 10^{-5}$$

$$R(7) = R(8) (1 + \alpha_1 (7-8) + \alpha_2 (7-8)^2)$$

$$R(7) = 105.3 (1 - (2.78964875 \times 10^{-3}) - (5.1935 \times 10^{-5}))$$

$$R(7) = 105.0007812 \Omega$$

PTC (positive temperature coefficient, sensor output goes up as the temperature goes up.)

Q1) Pressure sensor sensitivity (0.14mA/bar), @0bar=37mA, used in the range (0~50bar), use $R=120\Omega$ for conversion to volt: 2.5

a-Design signal conditioning circuit using 8bit ADC with voltage reference (0~4V).

b-Draw block diagram of the circuit.

c-Calculate sensor, I/V circuit output range?

D-What is the digital output if pressure is 14bar?

(14 marks)


e- Calculate the value of pressure if digital output is (11010100)₂.

Q2) using the following circuit to measure liquid level in a cylindrical tank, and using VFC with scale factor 6.2KHz/2.25V, with rate of 15sample/sec. a-Draw the block diagram.

b-Calculate the output voltage range (V_o), VFC output range, counter output range.


c- how many bits we need for the counter and controller digital inputs.

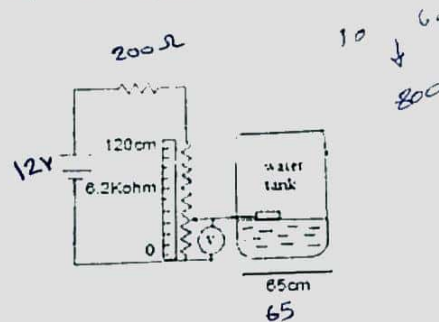d-what is the counter output will be, if the liquid level is 47cm, and what is the volume of the liquid? (10 marks)




Q3) Calculate the value of V_o , if the temperature in Kelvin.

(8 marks)

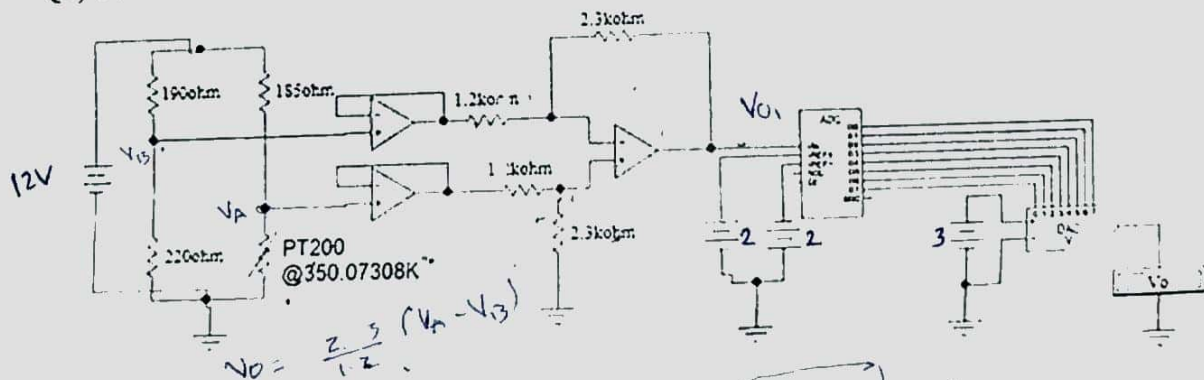

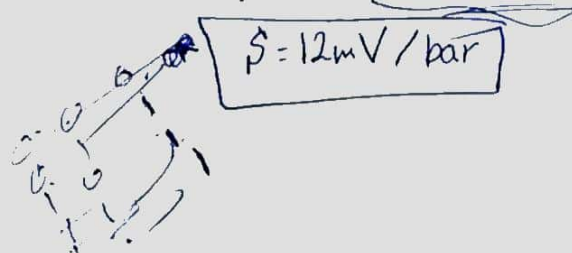Q4) Design circuit that operate heater if temperature is less than 32°C (using PT100), and open release valve if pressure is more than 10 bar, operate yellow LED if one of them is work. (8 marks)



Good luck

Fall 2020

midterm

Q1)

Sensor range (0 ~ 50 bar)

$$\text{Sensor current output range } (0 \times 0.14 + 37 \sim (50 \times 0.14) + 37) \\ = (37 \text{ mA} \sim 44 \text{ mA})$$

$$\text{Sensor voltage output range } = (37 \text{ mA} \times 120 \Omega \sim 44 \text{ mA} \times 120 \Omega) \\ = (4.44 \text{ V} \sim 5.28 \text{ V})$$

SC

$$4 = 5.28 \text{ M} + \text{offset}$$



$$0 = 4.44 \text{ M} + \text{offset}$$

$$\text{M} = 4.761905, \text{offset} = -21.1428582$$

$$V_{O2} = 4.761905 V_{O1} - 21.1428582$$

وسر صول التحقق

$$V_{O2} = 4.761905 (V_{O1} - 4.44)$$

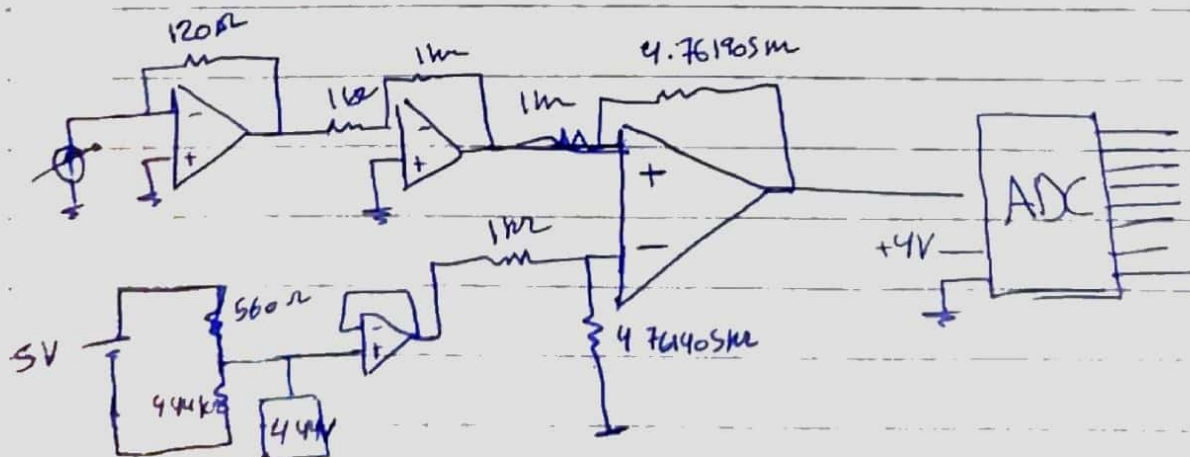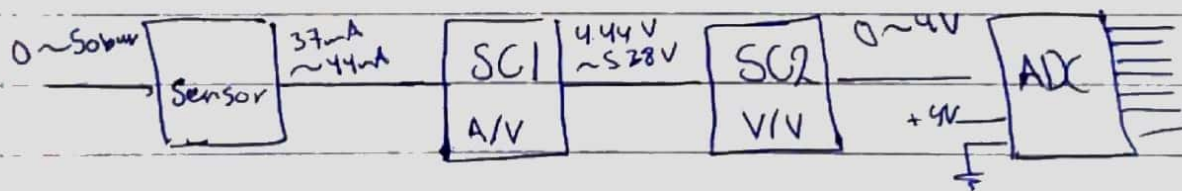

D @ 14 bar $I = (14 \times 0.14) + 37 = 38.96 \text{ mA}$

$$V_1 = 4.6752 \text{ V}, V_2 = 1.12 \text{ V}$$

For ADC $\Delta V = \frac{4-0}{2^8} = 0.015625 \text{ V}$

$$\text{Digital output} = \frac{1.12}{0.015625} = 71 = \boxed{01000111}$$

e) 11010100 $\rightarrow 212$ $V_2 = 212 \times \Delta V = 3.3125 \text{ V}$

$$V_1 = 5.135625 \text{ V} \rightarrow I = 42.796875 \text{ mA}$$

$$a = 41.40625 \text{ g}$$

Q2 tank height range (0 cm \sim 120 cm)

$$\text{voltage range (0 V \sim } 12 \times \frac{6.2}{6202} \text{)}$$

$$= (0 \text{ V} \sim 11.625 \text{ V})$$

$$\text{VFC } \frac{6.2 \text{ kHz}}{225 \text{ V}} = 2.7555556 \text{ kHz/V}$$

$$\text{VFC output range} = (0 \text{ kHz} \sim 32.033333 \text{ kHz})$$

$$T = \frac{1}{15} = 0.066667 \text{ sec}$$

counter output range = (0 ~ 2135)
= (000000000000 ~ 100001010111)

c) 12 bits

d) at 47cm ~~12cm~~ 120cm \rightarrow 11.625V

$$S = 0.096875 \text{ V/cm}$$

$$@ 47\text{cm} \quad V = 4.553125 \text{ V}$$

$$f = 12.546389 \text{ kHz}$$

$$\text{counter output} = 836 = 001101000100$$

$$Q3) \quad V_B = \frac{12 \times 220}{220 + 190} = 6.439024 \text{ V}$$

$$V_A \Rightarrow R_3 @ 176.7072667^\circ \text{C}$$

$$R_3 = 268.915834$$

$$V_A = 7.10922547 \text{ V}$$

$$V_{01} (\text{before ADC}) = \frac{2.3}{1.2} (V_A - V_B) = 1.284553 \text{ V}$$

for ADC $\Delta V = \frac{2 - (-2)}{2^8} = 0.015625V$

Digital output = $\frac{1.284553 + 2}{0.015625} = 216 = 11010010$

Digital input for DAC = 01001011 = 75

$\Delta V = \frac{3}{2^8} = 0.01171875V$

$V_0 = 75 \times \Delta V \rightarrow V_0 = 0.87890625V$

(24)

PT100 @ 32°C $R = (32 \times 39) + 100$


$R = 112.48\Omega$

use voltage divider $R = 200\Omega, V = 5V$

$V = 5 \times \frac{112.48}{112.48 + 200} = 1.799795V$


for the pressure sensor

@ 10 bar $V = 0.12V$

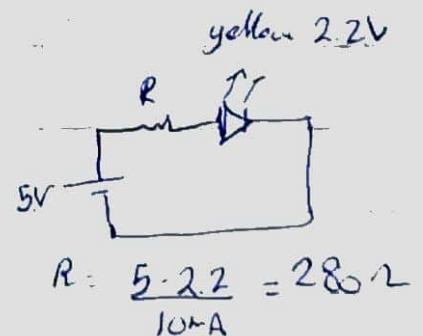

use $R = 330$

$I = 8.4848\mu A$

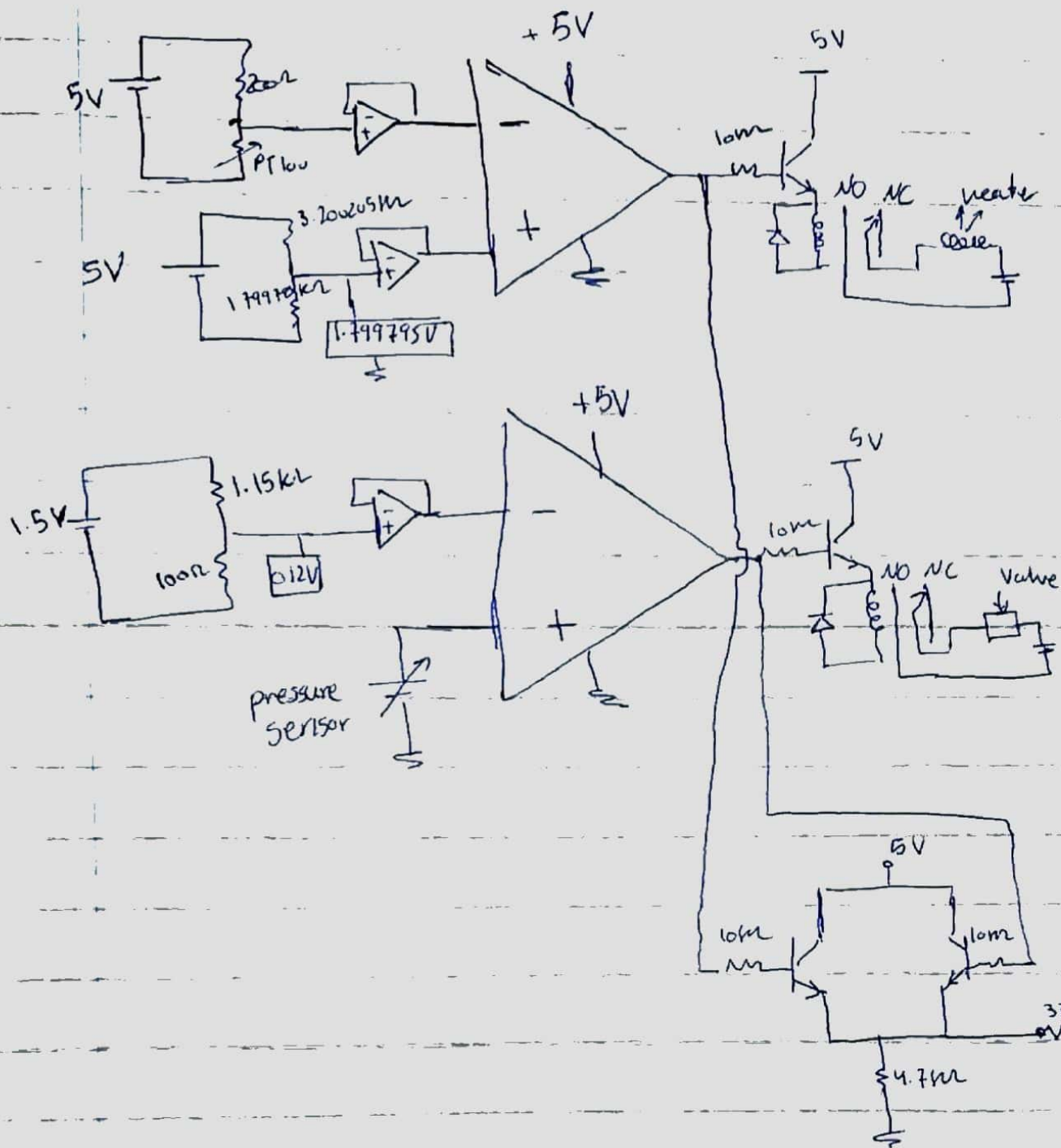

لو استغنت منه، أرجو منك
الدعوة بالرحمة لو الذي